
Homework #5


<u>Instructions:</u> Prepare your deliverables in clean letter size printer-quality papers with a high-contrast pencil (engineering pads are also accepted). Attach this assignment sheet as cover page, show all your work, and <u>box all your solutions</u>. All Matlab code needs to be published, with your name and date at the top of the script, and <u>all figures needs to have proper axis labeling and legends</u>. Homework assignments will be collected during class time on the due date. *Late homework or submission that do not strictly follow the provided instructions will not be accepted.*

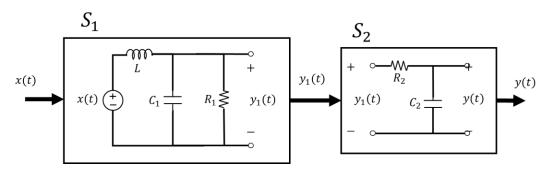- Homework problems not to be graded
 - o From textbook (Lathi):
 - Ch 2: 5-1
 - Ch 4: 1-3, 1-4
- Homework problems to be graded
- 1) Consider the following circuits connected in series. The input is the voltage x(t), the output to system S_1 is the voltage $y_1(t)$, and the output of system S_2 is the voltage y(t).




Let L = 0.01, $C_1 = 0.01$, $R_1 = 100$, $C_2 = 0.002$, and $R_2 = 50$.

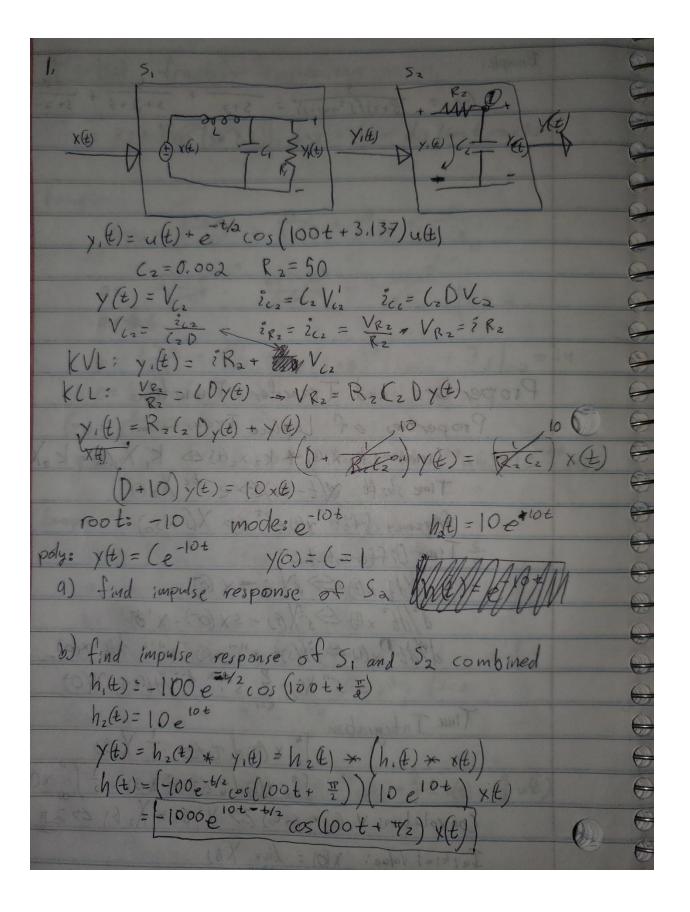- a. Find the impulse response of system S_2 .
- b. Find the impulse response of the combined system S from x(t) to y(t), using only the impulse response of S_1 and S_2 (the impulse response of system S_1 was found in HW #4).
- c. Find the zero-state response y(t) of combined system S to the unit step input x(t) = u(t). Show all your work.
- d. Compare the responses $y_1(t)$ and y(t) by plotting the signals in Matlab. Label all axes and include legends as needed to differentiate the signals. Note that S_2 is a low pass filter with bandwidth $^1/_{R_2C_2}$. What is the effect of adding S_2 on the system output y(t) of the combined system S?
- 2) Determine the internal stability and external (BIBO) stability of the following systems (*do not assume observability and/or controllability*)
 - (a) $(D^2 + 3D + 2)y(t) = (D + 3)x(t)$
 - (b) $(D^2 + 3D + 2)y(t) = (D + 1)x(t)$
 - (c) $(D^2 + D 2)y(t) = (D 1)x(t)$



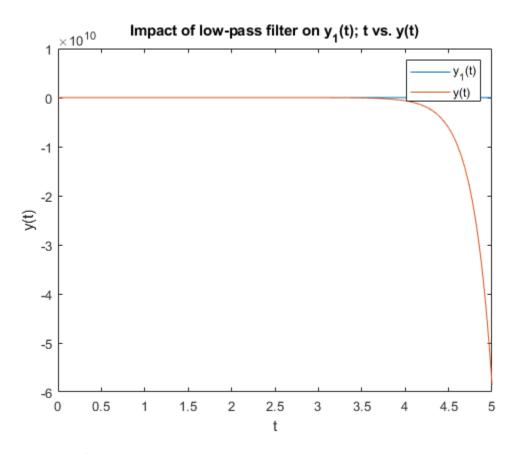c) find zero-state response y() of 5 h(b-T)=-1000e (100(t-T)+ 1/2) u(t-T) == 1000 e 9.5 t f # 1000 e 9.6 t cos (100(t-T) + 7/2) d T Convolution Integral # 12 = 4= -4.5, B=100, 0= 72, X=0 Φ=ton-(-//x)=1,48 rad
(05 (= + φ) = - e 9.5 t (100 t + = - φ) costo.09)-e-9.9+/100+0.09 160,45 y(t) = (-9,9e9.5t + 10cos (100t+0.09)) u(t)



The signal doesn't seem to oscillate at all anymore. It seems to oscillate when t<0 but go negative as soon as t>0. It also seems to drop off more starting at around t=4.

2.

