

TOTAL: ____/10

ECE 543: Introduction to Digital Systems

Homework #4

Due: Friday, November 5th, 2021 (6 P.M.)

Student Name: _____

Note:

- Please use these sheets as cover pages.
- Your work must be hand-written (no typing please).
- Homework must be submitted electronically through Canvas in a PDF format.

Part #1: Do the following problems from “Fundamentals of Digital Logic with Verilog Design” by Brown & Vranesic (3rd Edition).

Problems from Chapter 3:

3.3, 3.4, 3.5 (make sure to include carry-in and carry-out for each bit position)

Part #2: Solve the following problems.

1. Implement the following Boolean functions with an 8x1 MUX and external gates (AND, OR, and NOT).

(a)

A	B	C	F1
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

(b)

A	B	C	D	F2
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

2. Implement the Boolean functions given in Question 1 above with a 4x1 MUX and external gates (AND, OR, and NOT).

3. Implement the following Boolean function using a 1x8 DEMUX and external gates (AND, OR, and NOT).

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

4. Implement the following Boolean function using a 3x8 Decoder and external gates (AND, OR, and NOT).

$$F(A, B, C) = AC + \bar{B}$$

3.3

a.

b.

c.

a. 479

b. -231

c. -510

3.4

a. 00001001001 73

b. 01110110010 1906

c. 10000101111 -95

11100101110 -1630

b. 11110110110 73

10001001101 1906

01110100000 -95

00011010001 -1630

3.5

00110110
+ 01000101
01111011

01101010
+ 11011100
10000110
overflow

00110110
- 00101011
00001011

01110101
- 11101010
10011111

11010111
- 11101010
00011101
overflow


00110110
+ 11011101
00001011
overflow

01110101
+ 00101010
10011111

11010111
+ 00011101
11010111

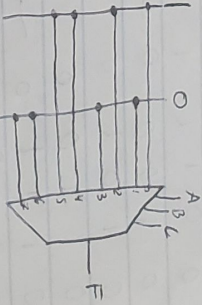
1. a) A B C F1

0 0 0 1
0 0 1 0
0 1 0 1
0 1 1 0
1 0 0 1
1 0 0 1
1 0 1 0
1 1 0 1



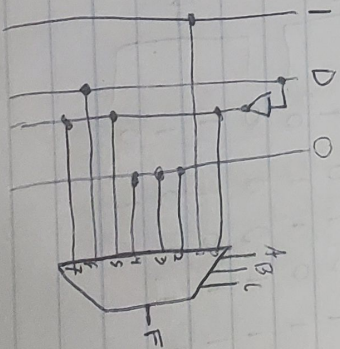
b) A B C D F2

0 0 0 0 1
0 0 0 1 1
0 0 1 0 1
0 0 1 1 1
0 1 0 0 1
0 1 0 1 1
0 1 1 0 1
0 1 1 1 1





2.

A	B	C	F1
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

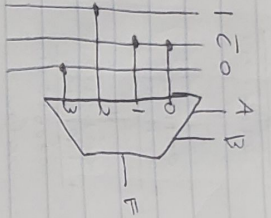


A	B	C	D	F2
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

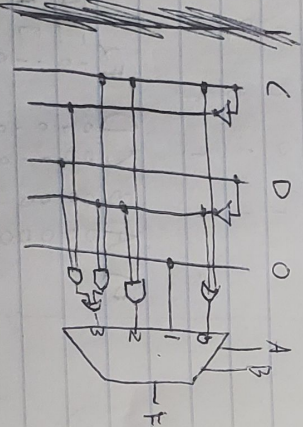
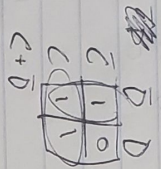


A	B	C	D	F2
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

$C\bar{D} + \bar{C}D$

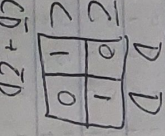

3.

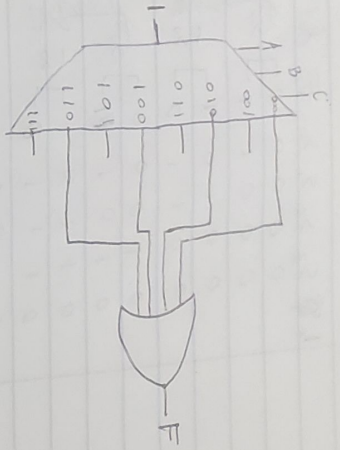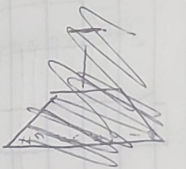

4.

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

