

|                       |
|-----------------------|
| <b>TOTAL: ____/10</b> |
|-----------------------|

ECE 543: Introduction to Digital Systems

Homework #5

**Due: Friday, December 10<sup>th</sup>, 2021 (6 P.M.)**

**Student Name:** \_\_\_\_\_

**Note:**

- **Please use these sheets as cover pages.**
- **Your work must be hand-written (no typing please).**
- **Homework must be submitted electronically through Canvas in a PDF format.**

**Part #1: Solve the following problems.**

1. (a) Design a synchronous counter using J-K FFs that has the following sequence: 000, 010, 101, 110, and repeat. The undesired (unused) states 001, 011, 100, and 111 must always go to 000 on the next clock pulse.  
  
(b) Redesign the counter of part (a) without any requirement on the unused states; that is, their NEXT states can be don't cares.
2. Design a synchronous, recycling, MOD-5 down counter that produces the sequence 100, 011, 010, 001, 000, and repeat. Use J-K flip-flops. Force the unused states to 000 on the next clock pulse.
3. Design a synchronous, recycling, MOD-7 up/down counter with J-K FFs. Use the states 000 through 110 in the counter. Control the count direction with input D (D = 0 to count up and D = 1 to count down).


**Part #2: Solve the following problems from “Fundamentals of Digital Logic with Verilog Design” by Brown & Vranesic (3<sup>rd</sup> Edition).**

Problems from Chapter 6:

6.3, 6.5, 6.15




1a.

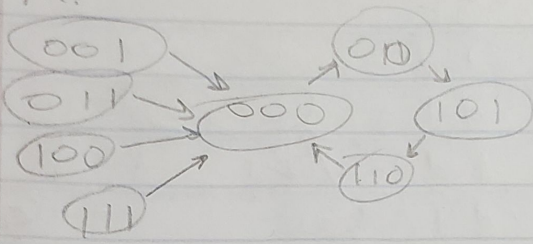


| Present state | Next state          | FF2   | FF1  | FF0  |
|---------------|---------------------|-------|------|------|
| $Q_2 Q_1 Q_0$ | $Q_2^+ Q_1^+ Q_0^+$ | $JK$  | $JK$ | $JK$ |
| 0 0 0         | 0 1 0               | 0 d 1 | d 1  | 0 d  |
| 0 0 1         | 0 0 0               | 0 d 0 | d d  | d 1  |
| 0 1 0         | 1 0 1               | 1 d 0 | 1 d  | 1 d  |
| 0 1 1         | 0 0 0               | 0 d d | 1 d  | 1    |
| 1 0 0         | 0 0 0               | d 1 0 | d 0  | d    |
| 1 0 1         | 1 1 0               | d 0 1 | d d  | d 1  |
| 1 1 0         | 0 0 0               | d 1 d | 1 0  | d    |
| 1 1 1         | 0 0 0               | d 1 d | 1 d  | 1    |

1b.

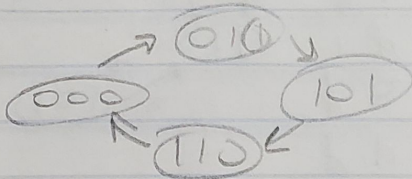

| $Q_2 Q_1 Q_0$ | $Q_2^+ Q_1^+ Q_0^+$ | $JK$ | $JK$ | $JK$ |
|---------------|---------------------|------|------|------|
| 0 0 0         | 0 1 0               | d 1  | 0 d  |      |
| 0 0 1         | d d d               | d d  | d d  |      |
| 0 1 0         | 1 0 1               | 1 d  | 1 d  |      |
| 0 1 1         | d d d               | d d  | d d  |      |
| 1 0 0         | d d d               | d d  | d d  |      |
| 1 0 1         | 1 1 0               | d 0  | 1 d  |      |
| 1 1 0         | 0 0 0               | d 1  | d 0  |      |
| 1 1 1         | d d d               | d d  | d d  |      |

2.

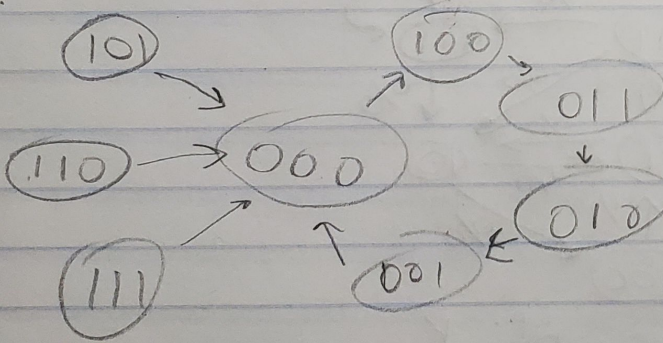

| $Q_2 Q_1 Q_0$ | $Q_2^+ Q_1^+ Q_0^+$ | $JK$ | $JK$ | $JK$ |
|---------------|---------------------|------|------|------|
| 0 0 0         | 1 0 0               | 1 d  | 0 d  | 0 d  |
| 0 0 1         | 0 0 0               | 0 d  | 0 d  | 1    |
| 0 1 0         | 0 0 1               | 0 d  | d 1  | 1 d  |
| 0 1 1         | 0 1 0               | 0 d  | d 0  | 1    |
| 1 0 0         | 0 1 1               | d 1  | 1 d  | 1 d  |
| 1 0 1         | 0 0 0               | d 1  | 0 d  | 1    |
| 1 1 0         | 0 0 0               | d 1  | d 1  | 0 d  |
| 1 1 1         | 0 0 0               | d 1  | d 1  | 1    |



