

ECE 401

Lab #3

Oct. 16

CMF

1. Plug correct wires and resistors into DMM, power supply, and bread board

2. record voltage drop

$$V_{R1} = 4.966V$$

3. Change DMM lead placement to measure

V_{R2}

4. record voltage drop

$$V_{R2} = 5.1V$$

5. Change DMM lead placement to measure V_{R3}

6. record voltage drop $V_{R3} = 4.96V$

7. ~~change input voltage~~ to change resistance to 10K, 20K, 30K

8. ~~repeat~~ measure V_{R1}, V_{R2}, V_{R3} again

9. record $V_{R1} = 2.494V, V_{R2} = 5.008V, V_{R3} = 7.467V$

10. Raise voltage to 20V DC, record $V_{R1} = 3.328V, V_{R2} = 6.681V, V_{R3} = 9.967V$

11. Lower voltage to 7.5V DC record $V_{R1} = 1.248V, V_{R2} = 2.506V, V_{R3} = 3.738V$

12. change to configuration 2 (parallel)

13. measure voltage drop $V_{R1,2,3} = 14.98V$


14. change resistances to 10K, 20K, 30K

15. measure voltage drop $V_{R1} = 14.98V$

16. add 1M Ω resistor to circuit

17. measure voltage drop 14.97

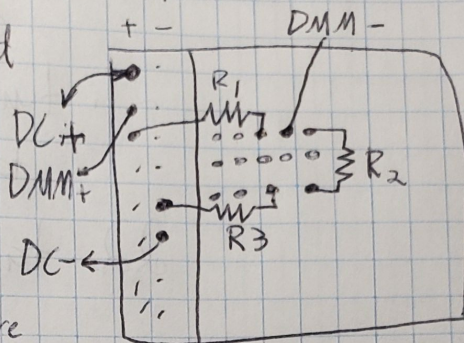18. unplug all ~~and~~ jumpers, leads, and resistors from bread board



19. Turn on function generator
and oscilloscope

20. Connect Coaxial to function generator
and oscilloscope

21. tune amplitude and frequency
to 19V_{ppk} and 60Hz

22. take picture with phone
of oscilloscope readout

23. Turn off both and disconnect
Coaxial cable

$$\% \text{ error} = \frac{\text{Calculated} - \text{measured}}{\text{Calculated}}$$