

## Lab 1: Review of Voltage and Current Measurement

Name: Nick SnyderDate: 1/30

Objective: The purpose of this lab is to refresh your memory on how to measure voltages and currents both (AC and DC) from an electrical circuit, how to use a DC power source, a function generator, and an oscilloscope.

## 1. Measuring DC voltage and current

- Construct the circuit in Figure 1 below, using the resistors available in the lab and a DC power source.

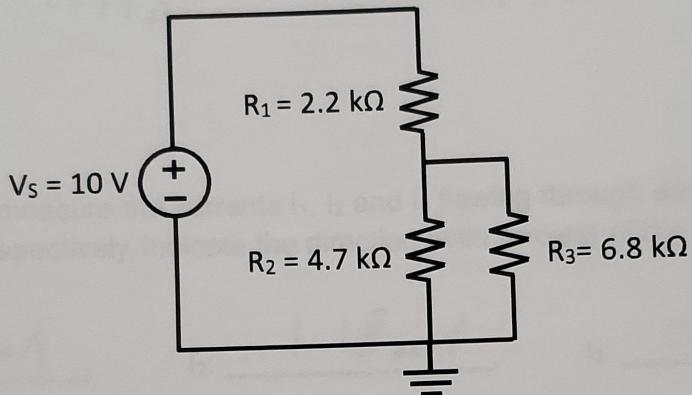


Figure 1

- Using the digital multimeter (DMM), measure the actual resistance values of the  $R_1$ ,  $R_2$  and  $R_3$ .

$$R_1: \underline{2.19 \text{ k}\Omega}, \quad R_2: \underline{4.64 \text{ k}\Omega}, \quad R_3: \underline{6.72 \text{ k}\Omega}$$

- What is the percentage of error between the measured resistance and the theoretical values as indicated in Figure 1?

$$R_1: \frac{0.45}{2.2} \times 100\% = 20.45\%, \quad R_2: \frac{0.17}{4.7} \times 100\% = 3.59\%, \quad R_3: \frac{0.17}{6.8} \times 100\% = 2.41\%$$


- Using the DMM, measure the voltages  $V_1$ ,  $V_2$  and  $V_3$  across each individual resistor  $R_1$ ,  $R_2$  and  $R_3$ , respectively. Indicate the polarity (+ and -) of the 3 measured voltages ( $V_1$ ,  $V_2$  and  $V_3$ ) in Figure 1.

$$V_1: \underline{4.44 \text{ V}}, \quad V_2: \underline{5.57 \text{ V}}, \quad V_3: \underline{5.57 \text{ V}}$$

- Using voltage division, calculate the theoretical values of the voltages  $V_1$ ,  $V_2$  and  $V_3$  across the resistors  $R_1$ ,  $R_2$  and  $R_3$ , respectively. Do the calculated values of  $V_1$ ,  $V_2$  and  $V_3$  match the measured values?

$V_1: 4.4V$ ,  $V_2: 5.6V$ ,  $V_3: 6.6V$

(Show your calculations below)

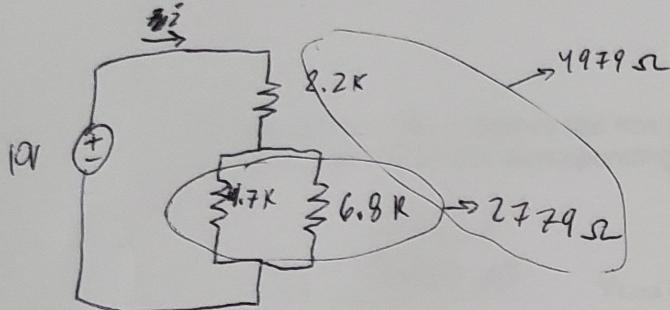

$$i = \frac{V}{R_{eq}} = \frac{10}{4979} = 0.002 A = 2mA$$

$$2.2k \cdot 2mA = 4.4V$$

$$10 - 4.4 = 5.6V$$


- Using the DMM, measure the currents  $I_1$ ,  $I_2$  and  $I_3$  flowing through each individual resistor  $R_1$ ,  $R_2$  and  $R_3$ , respectively. Indicate the direction (with arrows) of the 3 measured currents in Figure 1.

$I_1: 1.98mA$ ,  $I_2: 1.18mA$ ,  $I_3: 0.81mA$

- Using current division, calculate the theoretical values of the currents  $I_1$ ,  $I_2$  and  $I_3$  that should flow through the resistors  $R_1$ ,  $R_2$  and  $R_3$ , respectively. Do the calculated values of  $I_1$ ,  $I_2$  and  $I_3$  match the measured values?

$I_1: 2mA$ ,  $I_2: 1.19mA$ ,  $I_3: 0.82mA$

(Show your calculations below)

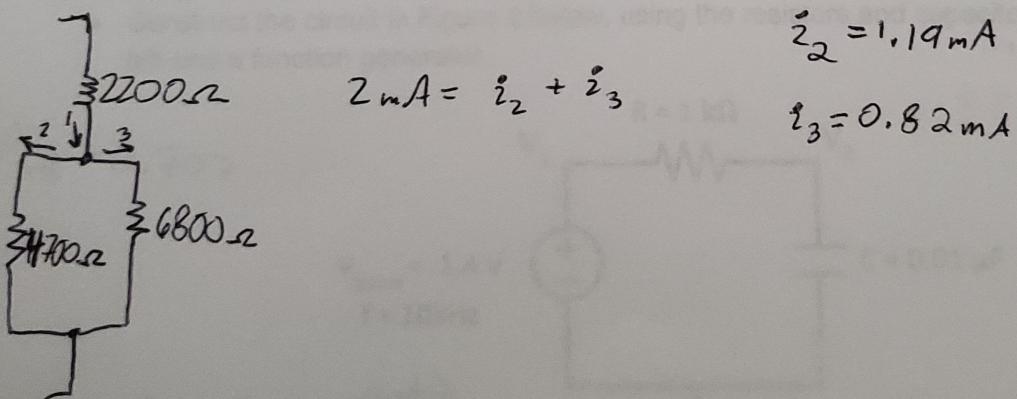

$$2mA = i_2 + i_3$$

$$i_2 = 1.19mA$$

$$i_3 = 0.82mA$$

Get TA's initial: B

113

2. Measuring AC voltage and current

- Replace the DC power source in Figure 1 with an AC power source using a function generator. Set the function generator to produce a sinusoidal voltage with a peak-to-peak amplitude of 2V and a frequency of 1kHz, i.e.  $V_s(t) = \sin(\omega t)$ . What is the rms (root-mean-square) value of  $V_s(t)$ ?

The rms value of the AC voltage source ( $V_{s,\text{rms}}$ ): 682 mV

*[Signature]*

- Using the DMM, measure the rms values of the voltages  $V_1$ ,  $V_2$  and  $V_3$ , and the rms values of  $I_1$ ,  $I_2$  and  $I_3$  for the corresponding resistors  $R_1$ ,  $R_2$  and  $R_3$ , respectively.

$$\begin{aligned} V_{1,\text{rms}} &: \frac{295 \text{ mV}}{\cancel{295 \text{ mV}}}, & V_{2,\text{rms}} &: \frac{370 \text{ mV}}{\cancel{370 \text{ mV}}} = & V_{3,\text{rms}} &: \frac{370 \text{ mV}}{\cancel{370 \text{ mV}}} \\ I_{1,\text{rms}} &: \frac{1.15 \text{ mA}}{\cancel{1.15 \text{ mA}}}, & I_{2,\text{rms}} &: \frac{0.68 \text{ mA}}{\cancel{0.68 \text{ mA}}} & I_{3,\text{rms}} &: \frac{0.47 \text{ mA}}{\cancel{0.47 \text{ mA}}} \\ I_{1,\text{rms}} &: \frac{115 \mu\text{A}}{\cancel{115 \mu\text{A}}}, & I_{2,\text{rms}} &: \frac{68 \mu\text{A}}{\cancel{68 \mu\text{A}}} & I_{3,\text{rms}} &: \frac{47 \mu\text{A}}{\cancel{47 \mu\text{A}}} \end{aligned}$$

Verify that  $V_{2,\text{rms}} = V_{3,\text{rms}}$  and  $V_{1,\text{rms}} + V_{2,\text{rms}} = V_{s,\text{rms}}$ . Also confirm that  $I_1 = I_2 + I_3$ .

$$68.5 + 47.5 = 116$$

Get TA's initial: *[Initials]*

3. Plotting the waveform with the oscilloscope

- Construct the circuit in Figure 2 below, using the resistors and capacitors available in the lab and a function generator.

$$V_{\text{rms}} = \sqrt{\text{peak}} \cdot 0.707$$

$$V_{s,\text{rms}} = 1.4 \text{ V}$$

$$f = 10 \text{ kHz}$$

$$x(t) = \cancel{x} + (x_0 - \cancel{x}) e^{-\frac{(t-t_0)}{RC}}$$


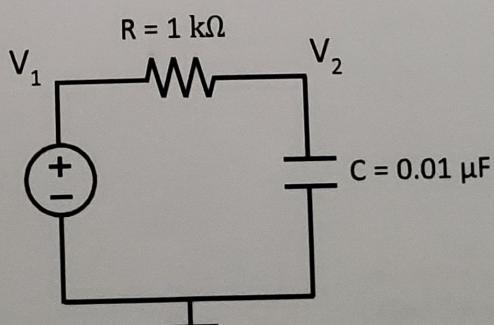


Figure 2

*[Signature]*

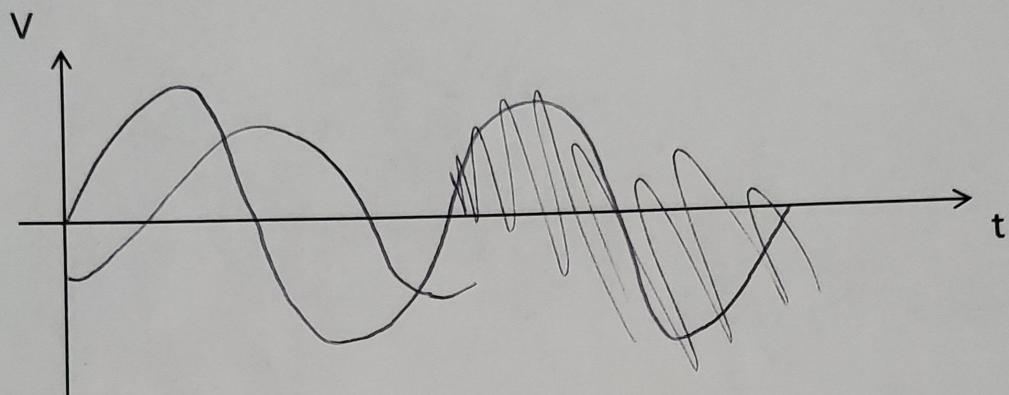- Using the oscilloscope display the waveform from the function generator ( $V_1$ ) in channel 1 and display the voltage across the capacitor ( $V_2$ ) in channel 2. In the axes provided below, draw 1 period of  $V_1$  and  $V_2$  on the same graph.



- Use the oscilloscope to measure the phase shift between the function generator signal and the capacitor voltage.

Phase shift: 27.0 degrees =  $0.47$  radians

- Using the DMM, measure the RMS value of the capacitor voltage ( $V_{2,\text{rms}}$ )

$$V_{2,\text{rms}} = \underline{\underline{361 \text{ mV}}} \quad 361 \text{ mV}$$

- What is the theoretical value of  $V_{2,\text{rms}}$ ? Does it match the measured value?

$$V_{2,\text{rms}} = \underline{\underline{361 \text{ mV}}}$$

(Show calculation below)

Get TA's initial:

D  
13 |