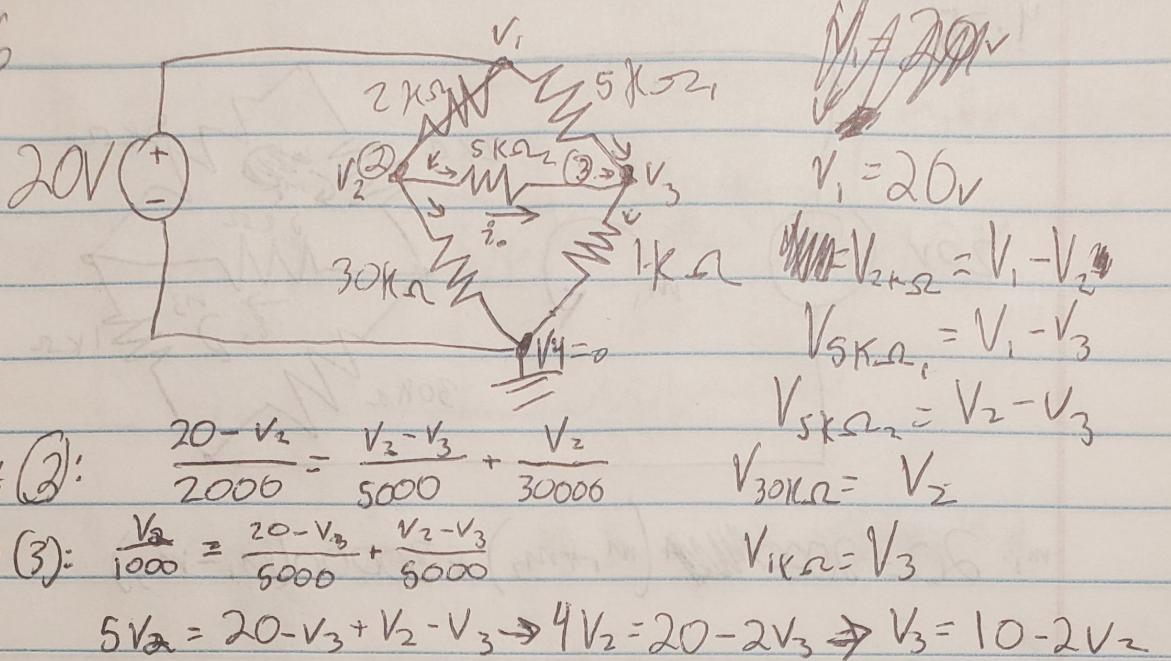


4.26



$$KCL \text{ at (2)}: \frac{20 - V_2}{2000} = \frac{V_2 - V_3}{5000} + \frac{V_2}{30000}$$

$$KCL \text{ at (3)}: \frac{V_2}{1000} = \frac{20 - V_3}{5000} + \frac{V_2 - V_3}{5000}$$

$$5V_2 = 20 - V_3 + V_2 - V_3 \Rightarrow 4V_2 = 20 - 2V_3 \Rightarrow V_3 = 10 - 2V_2$$

$$\frac{20 - V_2}{2} = \frac{V_2 - (10 - 2V_2)}{5} + \frac{V_2}{30}$$

$$10 - \frac{1}{2}V_2 = \frac{V_2 - 10 + 2V_2}{5} + \frac{V_2}{30} \quad 10 - \frac{1}{2}V_2 = \frac{1}{5}V_2 - 2 + \frac{2}{5}V_2 + \frac{V_2}{30}$$

$$10 - \frac{1}{2}V_2 = \frac{6}{30}V_2 + \frac{12}{30}V_2 + \frac{1}{30}V_2 + \frac{15}{30}V_2$$

$$V_3 = 10 - 2(7.1) = -4.2V \quad 8 = \frac{34}{30}V_2 \Rightarrow V_2 = 7.1V$$


$$V_{5k\Omega} = V_2 - V_3 = 7.1 + (-4.2) = 11.3V$$

$$i = \frac{V}{R}$$

$$i_0 = \frac{11.3}{8000} = 1.413mA$$

Ampere's Law: $\oint B \cdot d\ell = \mu_0 I_{ext}$

4.35

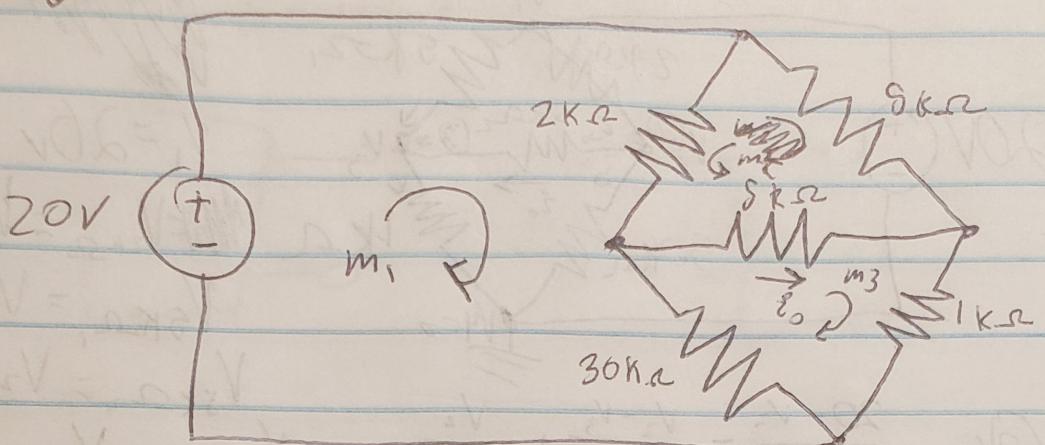

$$m_1: 20 = 2000(m_1 + m_2) + 30000(m_1 - m_3)$$

$$m_3: 0 = 5000(m_2 + m_3) + 1000m_3 + 30000(m_3 - m_1)$$

~~$$0 = 25000m_2 + 30000m_3$$~~

$$m_2: 0 = 5000(m_2 + m_3) + 5000m_2 + 2000(m_1 + m_2)$$


$$32000m_1 + 2000m_2 - 30000m_3 = 20$$

$$-30000m_1 + 5000m_2 + 36000m_3 = 0$$

$$2000m_1 + 12000m_2 + 5000m_3 = 0$$

$$\begin{array}{l} \left[\begin{array}{ccc|c} m_1 & 32000 & 2000 & -30000 & 20 \\ m_2 & -30000 & 5000 & 36000 & 0 \\ m_3 & 2000 & 12000 & 5000 & 0 \end{array} \right] \begin{array}{l} m_1 = 5,5mA \\ m_2 = -3mA \\ m_3 = 5mA \end{array} \\ \boxed{I_o = m_2 + m_3 = 2mA} \end{array}$$

4.50

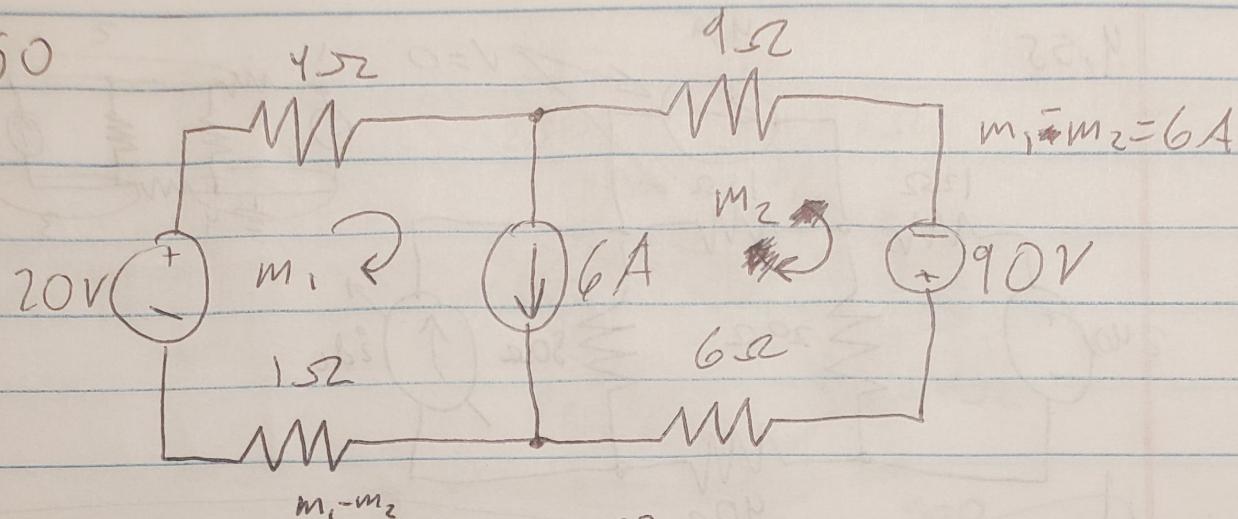

$$m_1: 20 = 4m_1 + \cancel{16} + 1m_1 \quad \cancel{16} = 5m_1 \quad m_1 = 2.8 \text{ A}$$

$$m_2: 90 = 6m_2 - \cancel{10} + 9m_2 \quad \cancel{10} = 15m_2 \quad m_2 = 6 \text{ A}$$

~~total~~

$$90 = 15m_2 - m_1 + m_2 \quad m_1 = \frac{90 - m_2}{16}$$

$$20 = 5m_1 + m_1 - m_2 \quad \cancel{m_1} \quad m_2 = 6m_1 - 20$$

$$m_1 = \frac{90 - (6m_1 + 20)}{16} \quad \frac{110}{16} - \frac{m_1}{16} = m_1 \quad 110 - m_1 = 16m_1$$

$$110 = 17m_1 \quad m_1 = \frac{110}{17} = 6.5 \text{ A}$$

$$m_2 = \frac{660}{17} - 20 = 18.8 \text{ V}$$

$$\cancel{V} = IR \quad V = I R$$

$$V_{1\Omega} \quad 26 \text{ V} \quad 6.5 \text{ A} \quad 169 \text{ W}$$


$$V_{6\Omega} \quad 6.5 \text{ V} \quad 6.5 \text{ A} \quad 42.25 \text{ W}$$

$$V_{4\Omega} \quad 169.2 \text{ V} \quad 18.8 \text{ A} \quad 3121 \text{ W}$$


$$V_{9\Omega} \quad 112.8 \text{ V} \quad 18.8 \text{ A} \quad 2121 \text{ W}$$

5513.25 W

9.55

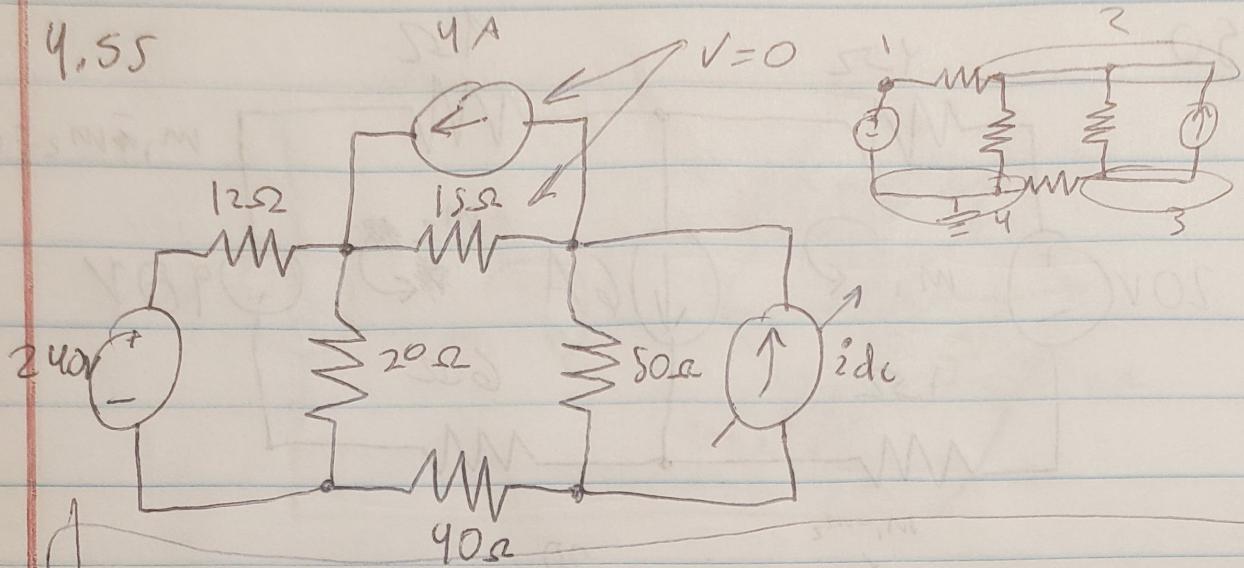

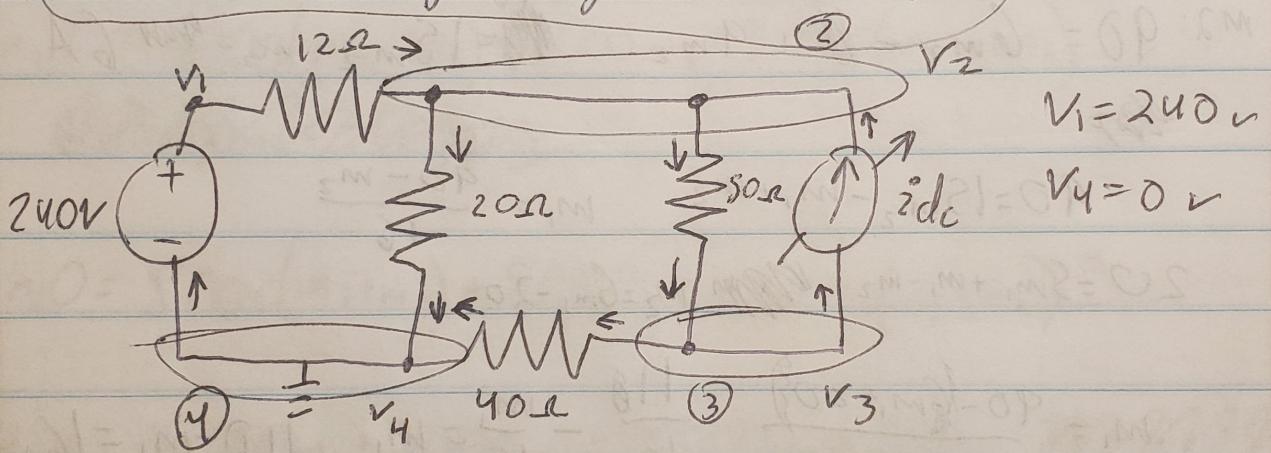a) Model - ~~By Nodal Analysis we can use node voltage because it has 4 easily recognizable nodes.~~



$$\textcircled{2}: \frac{240 - V_2}{12} + i_{dc} = \frac{V_2}{20} + \frac{V_2 - V_3}{50}$$

$$-\frac{8}{50}V_3 - \frac{960}{6000} = -\frac{800}{6000} - \frac{120}{6000}V_2 + \frac{1}{12}V_2 - \frac{1}{20}V_2 + \frac{V_2}{50} + \frac{1}{50}V_3 + i_{dc} = -20$$

$$\textcircled{3}: \frac{V_2 - V_3}{50} = \frac{V_3}{40} + i_{dc} \quad \underbrace{\frac{1}{50}V_2 - \frac{1}{50}V_3 - \frac{1}{40}V_3 - i_{dc}}_{-\frac{9}{200}V_3} = 0$$


$$\textcircled{4}: \frac{V_2}{20} + \frac{V_3}{40} = \frac{240 - V_2}{12} \quad \frac{1}{12}V_2 + \frac{1}{40}V_3 + \frac{1}{12}i_{dc} = 20$$

$\frac{1}{12}$	$\frac{1}{40}$	$\frac{1}{12}$	20
$\frac{1}{50}$	$-\frac{9}{200}$	-1	0
$-\frac{8}{50}$	$\frac{1}{50}$	1	-20

$V_2 = -0.0882V$
 $V_3 = 1.2941V$
 $i_{dc} = -0.06A$

b)

4.56

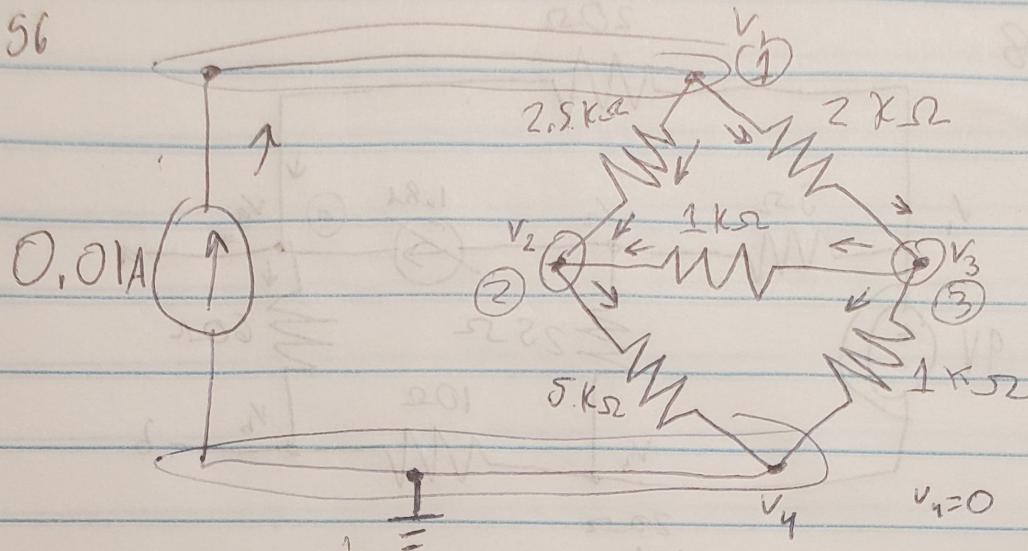

(a) node-voltage because I don't have a defined voltage

$$\textcircled{1}: 0.01 = \frac{V_1 - V_2}{2500} + \frac{V_1 - V_3}{2000} \Rightarrow \frac{V_1}{2500} + \frac{V_1}{2000} - \frac{V_2}{2500} - \frac{V_3}{2000} = 0.01$$

$$\textcircled{2}: \frac{V_1 - V_2}{2500} + \frac{V_3 - V_2}{1000} - \frac{V_2}{5000} = 0 \Rightarrow \frac{V_1}{2500} - \frac{16V_2}{10000} - \frac{V_3}{2000} = 0$$

$$\textcircled{3}: \cancel{\frac{V_1 - V_3}{2000}} + \frac{V_1}{2000} + \frac{V_3}{2000} - \frac{V_3 - V_2}{1000} - \frac{V_3}{1000} = 0 \Rightarrow \frac{V_1}{2000} + \frac{V_2}{1000} - \frac{3V_3}{2000} = 0$$

$\frac{9}{10000}$	$-\frac{1}{2500}$	$-\frac{1}{2000}$	0.01	$V_1 = 11.7409V$
$\frac{1}{2500}$	$-\frac{1}{625}$	$-\frac{1}{2500}$	0	$V_2 = 3.4413V$
$-\frac{1}{2000}$	$\frac{1}{1000}$	$-\frac{3}{2000}$	0	$V_3 = -1.6194V$

$$(b) P_{H1K\Omega} = \frac{V^2}{R} = \frac{(V_3 - V_2)^2}{R} = \frac{25.61}{1000} = 0.02561W$$

c) no, I would sum the power dissipated by each resistor

$$P_{R2.5k\Omega} = \frac{(V_1 - V_2)^2}{R} = \frac{68.68}{2500} = 0.02755W$$



$$P_{R2k\Omega} = \frac{(V_1 - V_3)^2}{R} = \frac{178.5}{2000} = 0.08925W$$

$$P_{R5k\Omega} = \frac{V_2^2}{R} = \frac{11.84}{5000} = 0.00237W$$

$$P_{R1k\Omega} = \frac{V_3^2}{R} = \frac{2.622}{1000} = 0.00262W$$


$$d) P_S = 0.12179W$$

4.78

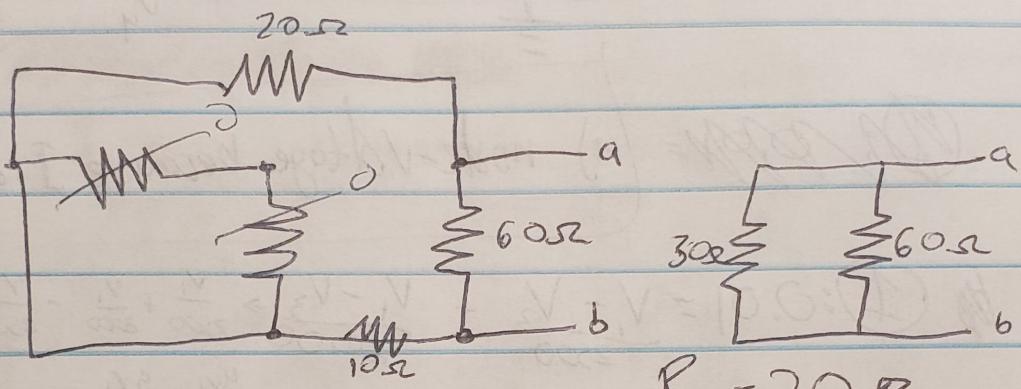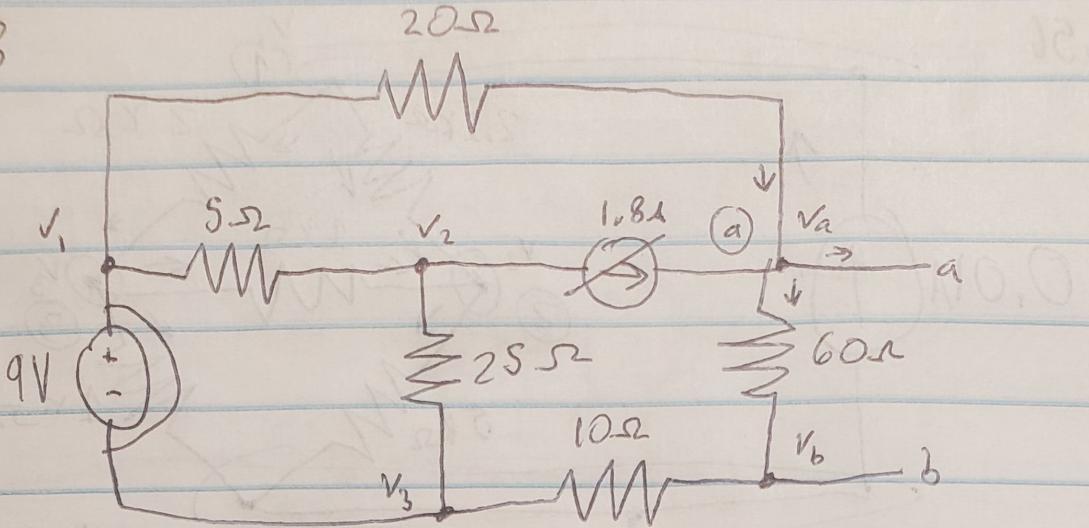

$$R_z = 20\Omega$$
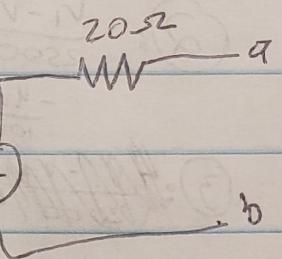
$$\textcircled{a}: 1.8 + \frac{9-V_a}{20} = i_a + \frac{V_a - V_b}{60}$$



$$V_{PONT} \text{ II} = V_{10.0}$$

$$V_{CIRCUIT} = 0$$

$$V_{HPII} = 1 - V$$

$$w 10 \cdot 50,0 = 50,0 \quad (V - V)$$

