

## Lab 3: Diodes

Name: Nick SnyderMajor: CE**Objective:**

- To understand and experimentally verify the current-voltage (I-V) characteristics of a diode.
- To build a voltage limiter circuit and understand the state of each diode during operation.
- To assemble, test, and understand the half-wave rectifier circuit using diodes.

**1. I-V Characteristics of a Silicon Diode**

- Construct the circuit in Figure 1 below using the 1N4148 Silicon diode. Note that the polarity band indicates the n-side of the diode. Please refer to the data sheet for the diode specifications.  $V_s$  is connected to the DC power supply. Use the digital multimeter to measure the voltage  $V_o$  between the diode and the resistor.

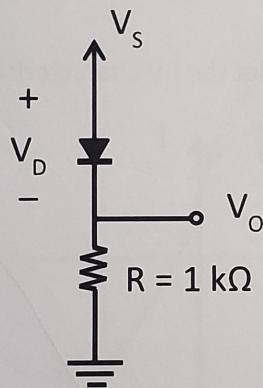


Figure 1

- Vary the DC voltage  $V_s$  from -2 V to 2 V and complete the following table.

Table 1


$V_s$ [V]	$V_o$ [V]	$V_D$ [V]	$I_D$ [mA]
-2	0 V	-2 V	0
-1	0 V	-1 V	0
0	0 V	-13 mV	0
0.2	360 μV	205 mV	0.27 μA
0.4	13 mV	389 mV	13.21 μA
0.5	51 mV	457 mV	46.38 μA

0.6	0.111 V	0.495 V	104 mA
0.7	0.16 V	0.521 V	167 mA
0.8	0.27 V	0.540 V	248 mA
0.9	0.353 V	0.553 V	321 mA
1.0	0.446 V	0.564 V	400 mA
1.2	0.623 V	0.581 V	572 mA
1.4	0.811 V	0.593 V	738 mA
1.6	0.997 V	0.604 V	912 mA
1.8	1.18 V	0.611 V	1.09 mA
2.0	1.38 V	0.620 V	1.26 mA

- At what  $V_D$  does the diode start to conduct?

$$V_0 = 0.5 V$$

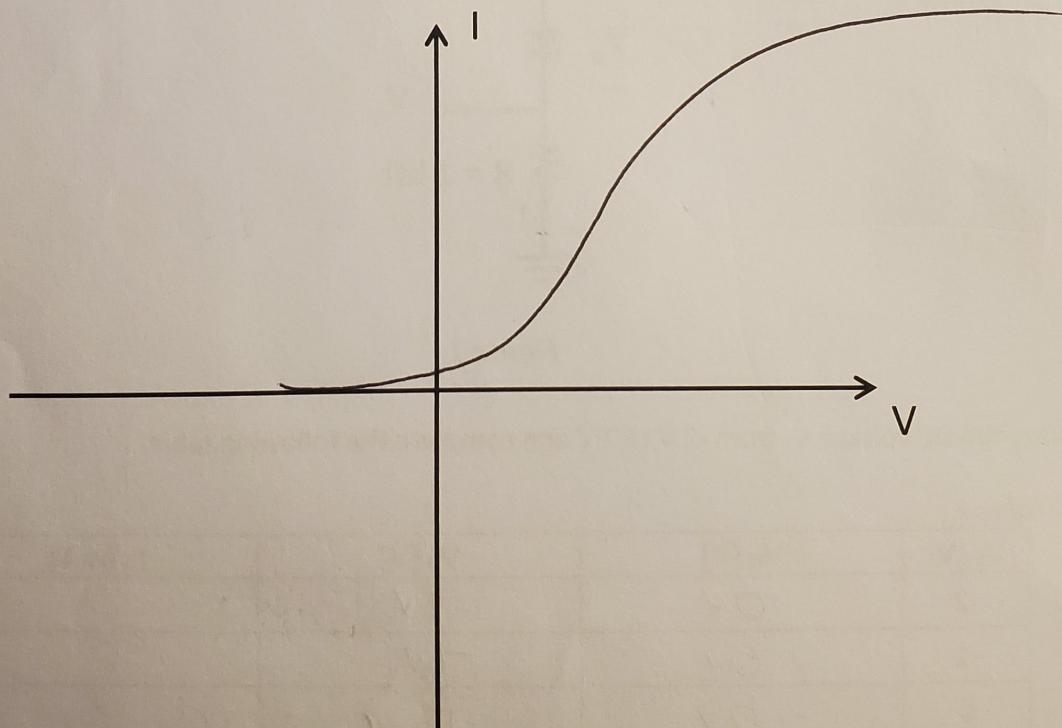- Using the data from tables 1 and 2, plot the I-V characteristics in the axes provided below.



Get TA's initial:

Q  
3/07

## 2. Voltage Limiter

- Construct the circuit in Figure 2. Using a function generator, produce a sine wave at  $V_s(t)$  with 1kHz frequency and 2 V amplitude. Use channel 1 of oscilloscope to display  $V_s$  and channel 2 to display  $V_o$  on the scope.


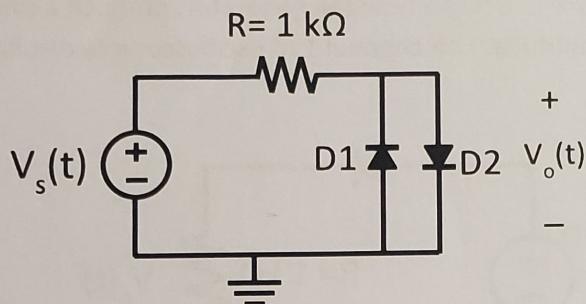


Figure 2

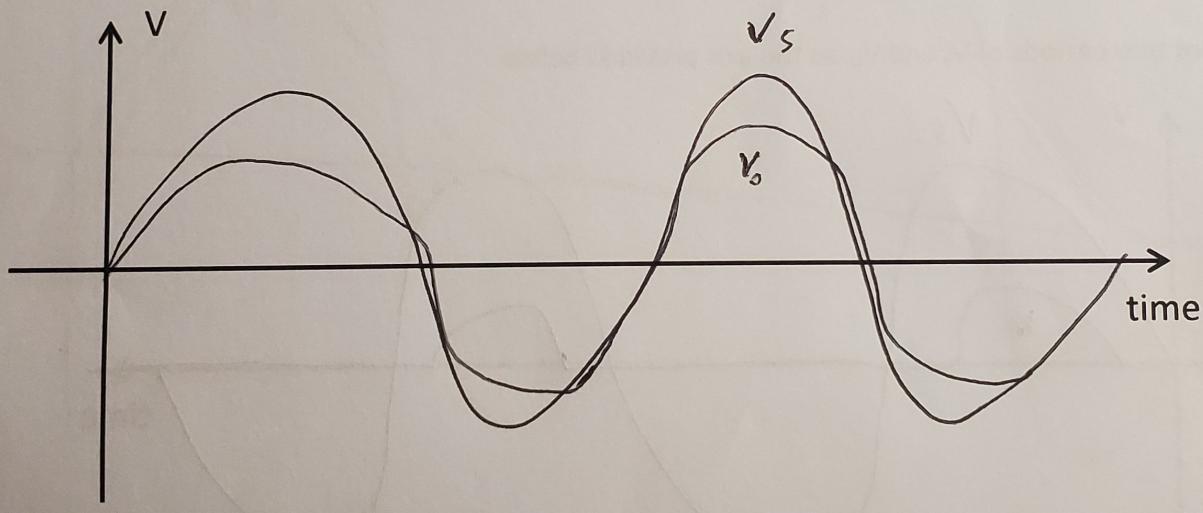- Plot two periods of  $V_s$  and  $V_o$  on the axis provided below.



- What are the voltage ranges of  $V_s(t)$  for which the following diode conditions apply? Complete the table below.

D1	D2	Range of $V_s(t)$
ON	ON	short circuit
ON	OFF	both 8 mA
OFF	ON	
OFF	OFF	open circuit

Get TA's initial:

✓  
C312X

### 3. Half-Wave Rectifier

- Construct the circuit in Figure 2. Using a function generator, produce a sine wave at  $V_s(t)$  with 1kHz frequency and 2 V amplitude. Use channel 1 of oscilloscope to display  $V_s$  and channel 2 to display  $V_o$  on the scope.


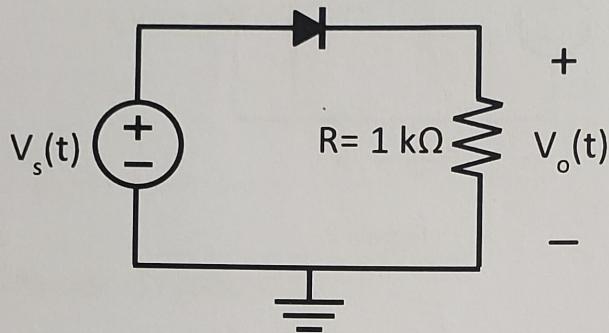


Figure 3

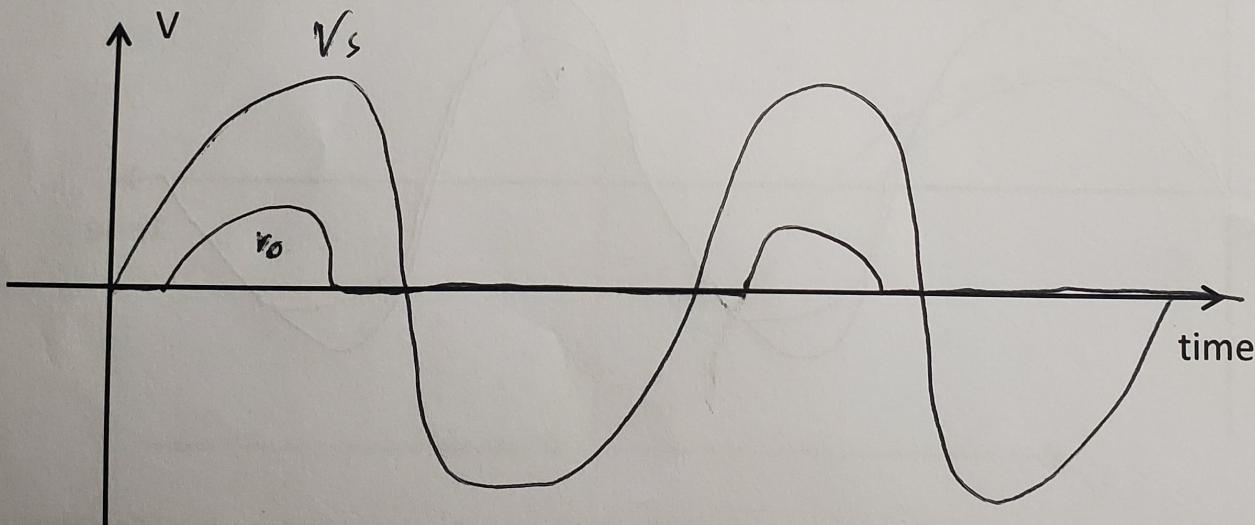- Plot two periods of  $V_s$  and  $V_o$  on the axis provided below.



- What is the peak voltage of  $V_o$ ? How does it compare to the peak voltage of  $V_s$ ?


$$V_{oP} = \cancel{1.02V} \quad 1.02V$$

$$V_{sP} = \cancel{2V} \quad 2V$$

- From Figure 2, add a  $1 \mu\text{F}$  capacitor in parallel with the  $1\text{K}\Omega$  resistor and plot the resulting  $V_o$  on the above axis.
- What is the maximum, minimum and the magnitude of the "ripple" voltage?

Get TA's initial:

Car  
3/27

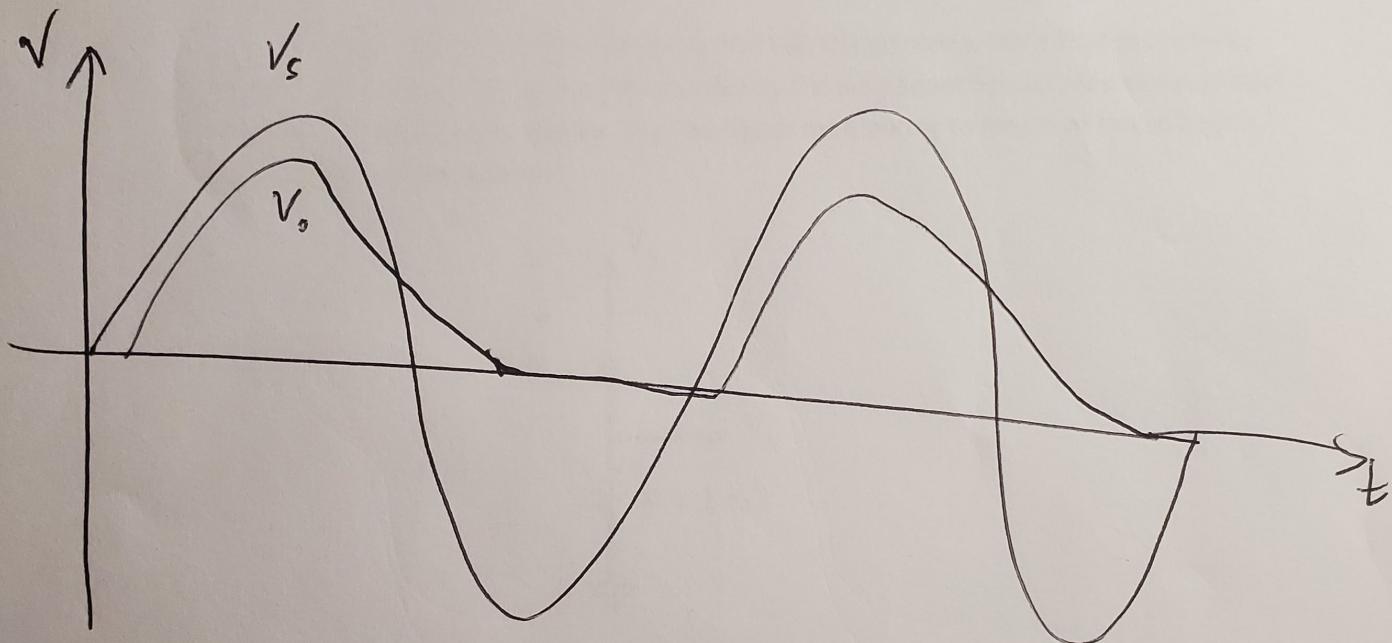

max  $920 \text{ mV}$

min  $-440 \text{ mV}$

mag  $1, 3 \text{ V}$