

ECE 541: Electric Circuits

Laboratory Exercise #2

Weeks of 10/03/22 (Group A) and 10/10/22 (Group B)

Name: Nick Snyder

Date: 10/03/22

Objective

To introduce the student to construct and analyze voltage and current divider circuits.

Voltage Divider Circuit

1. Connect the series circuit as shown in Figure 1

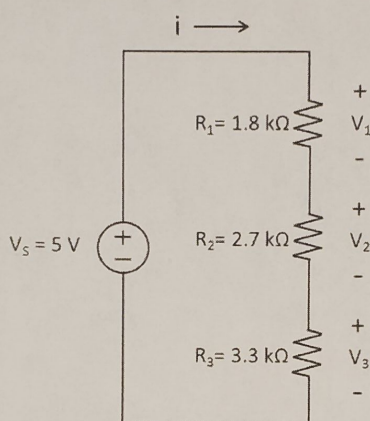


Figure 1: Series Circuit

$$\frac{5}{7,800} = 0.64\text{ mA}$$

2. (Pre-Lab) Use voltage division principle to calculate the voltages V_1 , V_2 , and V_3 in figure 1 (show your calculations).

$$0.64 \cdot 1.8 = 1.15$$

$$0.64 \cdot 2.7 = 1.73$$

$$0.64 \cdot 3.3 = 2.12$$

$$V_1: \underline{1.15}$$

$$V_2: \underline{1.73}$$

$$V_3: \underline{2.12}$$

3. (Pre-Lab) Calculate the current in figure 1 (show your calculations).

$$R_{eq} = \frac{7800 \Omega}{1} = 7800 \Omega$$

i: 0.64 mA

$$\frac{V}{R} \rightarrow \frac{5}{7800} = 0.64 \text{ mA}$$

4. Measure the actual value of the three resistors in the circuit:

R1: $1.76 \text{ k}\Omega$

R2: $2.69 \text{ k}\Omega$

R3: 3.25

5. Measure the voltage between the nodes in the circuit:

V1: 1.15

V2: 1.75

V3: 2.11

6. Measure the current through the resistors in the circuit:


i: 0.64 mA

7. Do the measured voltage and current values agree with the theoretical values according to Ohm's Law and the voltage divider rule? Which resistor has the largest voltage drop across it?

yes the most resistive resistor ($3.3 \text{ k}\Omega$)
has the largest voltage drop
across it

Current Divider Circuit

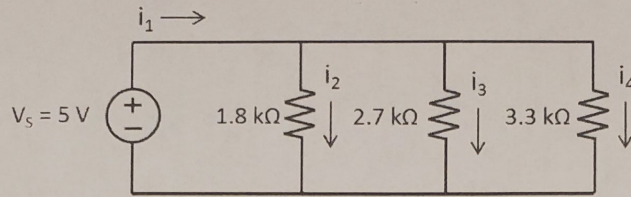1. Connect the parallel circuit as shown in Figure 2.



$$R_{eq} = 813.7\Omega$$

Figure 2. Parallel Circuit

2. (Pre-Lab) Using the current division principle, calculate each current in figure 2 (show calculations).

$$\begin{array}{llll} 6.1\text{ mA} & 2.7\text{ mA} & & \\ I_1: \underline{\quad\quad\quad} & I_2: \underline{\quad\quad\quad} & I_3: \underline{1.85\text{ mA}} & I_4: \underline{1.51\text{ mA}} \end{array}$$

3. (Pre-Lab) What is the expected voltage across each of the resistors?

$$5\text{ V}$$

4. Measure the currents in the parallel circuit. Make sure to connect the multimeter in series with each resistor.

$$\begin{array}{llll} 6.21\text{ mA} & 2.68\text{ mA} & 1.79\text{ mA} & 1.49\text{ mA} \\ I_1: \underline{\quad\quad\quad} & I_2: \underline{\quad\quad\quad} & I_3: \underline{\quad\quad\quad} & I_4: \underline{\quad\quad\quad} \end{array}$$

5. Do the measured values of the current match the calculated ones?

yes, pretty close

Series and Parallel Circuit

1. Connect the series and parallel circuit as shown in Figure 3.

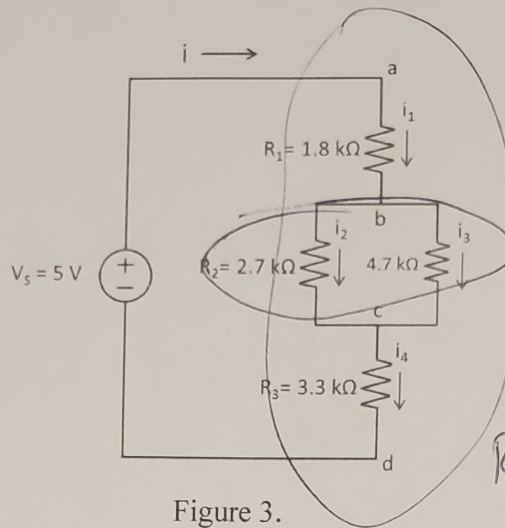


Figure 3.

$$V_{R_1} = 1.32 \text{ V}$$

$$R_{eq1} = 1714.4 \Omega$$

$$R_{eq2} = 6814.9 \Omega$$

2. (Pre-lab) Calculate the currents in the circuit (show calculations). Use the measured values of the resistors.

~~$$I_1 = I_4 = \frac{5}{6815} = 0.73 \text{ mA}$$~~

$$5 - 1.32 = 3.68 \text{ V}$$

$$I_1 = I_4 = \frac{5}{6815} = 0.73 \text{ mA}$$

~~$$\frac{3.68}{2700} = 1.36 \text{ mA}$$~~

$$1800 + \frac{1}{\frac{1}{2700} + \frac{1}{4700}} + 3300 = 6815 \Omega$$

~~$$\frac{3.68}{4700} = 0.78 \text{ mA}$$~~

$$I_2 \cdot 2700 = I_3 \cdot 4700$$

~~$$\frac{3.68}{1715} = 2.15 \text{ mA}$$~~

$$0.46 \text{ mA} \quad 0.27 \text{ mA}$$

$$I_1: 0.73 \text{ mA}$$

$I_2:$

$I_3:$

$$I_4: 0.73 \text{ mA}$$

3. (Pre-Lab) Calculate the voltages between the nodes in the circuit (show calculations). Use the measured values of the resistors.

$$0.73 \text{ mA} \cdot 1800 \Omega$$

~~0.73 mA~~

$$V = IR$$

$$0.73 \text{ mA} \cdot 3300 \Omega$$

$$0.73 \text{ mA} \cdot 1715 \Omega$$

$$0.73 \text{ mA} \cdot 6815 \Omega$$

$$V_{ab}: 1.32 \text{ V} \quad V_{bc}: 1.25 \text{ V} \quad V_{cd}: 2.41 \text{ V} \quad V_{ad}: 4.97 \text{ V}$$

4. Measure the currents in the circuit (Make sure to connect the multimeter in series):

$$I_1: 0.73 \text{ mA} \quad I_2: 0.46 \text{ mA} \quad I_3: 0.27 \text{ mA} \quad I_4: 0.73 \text{ mA}$$

5. Measure the voltages between nodes in the circuit:

$$V_{ab}: 1.31 \text{ V} \quad V_{bc}: 1.27 \text{ V} \quad V_{cd}: 2.42 \text{ V} \quad V_{ad}: 5.01 \text{ V}$$

6. Do the calculated values of current and voltage match the measured values of current and voltage?

yes, pretty close