

## Lab 5: Three-Terminal Devices – MOSFETs

Name: Nick SnyderDate: 5/2/23**Objective:**

- To understand and experimentally determine the I-V characteristics of an n-channel MOSFET.
- To build and understand the operation of a CMOS (Complementary MOSFET) logic inverter.

**1. N-channel MOSFET (NMOS)**

- Assemble the circuit in Figure 1(a) using a 2N7000 n-channel MOSFET. Use channel 1 of the DC supply to power  $V_{GS}$  and channel 2 for  $V_{DD}$ .
- For a fixed value of  $V_{GS}$ , adjust the  $V_{DD}$  value until the desired  $V_{DS}$  is obtained in order to measure the current ( $I_D$ ) through the MOSFET. Use the table below.

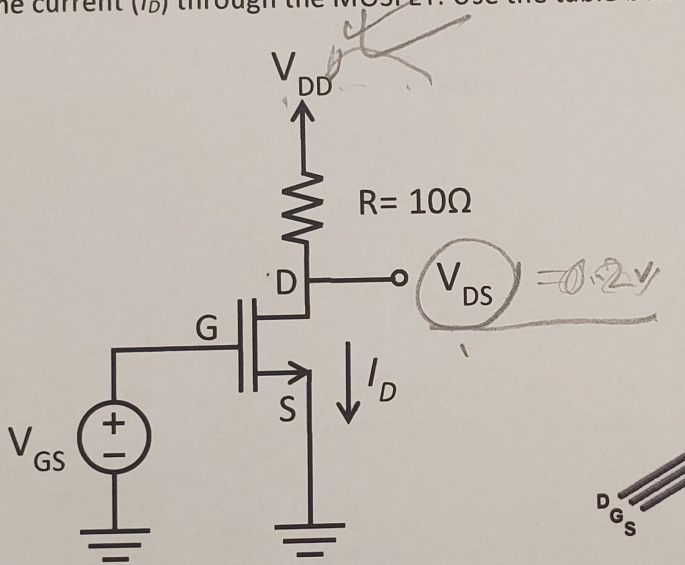


Figure 1(a)


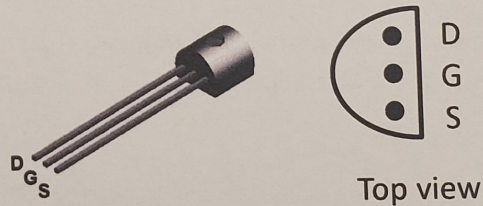


Figure 1(b)

	<u><math>V_{DS} = 0.2V</math></u>		$V_{DS} = 0.5V$		$V_{DS} = 1V$		$V_{DS} = 1.5V$		$V_{DS} = 2V$	
	$V_{DD}$	$I_D$	$V_{DD}$	$I_D$	$V_{DD}$	$I_D$	$V_{DD}$	$I_D$	$V_{DD}$	$I_D$
$V_{GS} = 1V$	0.44	0.024	0.86	0.038	1.42	0.043	1.5	0	2	0
$V_{GS} = 2V$	0.71	0.052	1.64	0.116	2.76	0.181	1.5	0.099	2	0.098
$V_{GS} = 3V$	0.83	0.063	2.02	0.154	3.65	0.259	2.05	0.055	2.53	0.053
$V_{GS} = 4V$	0.90	0.71	2.08	0.163	3.25	0.225	4.28	0.282	5.04	0.309

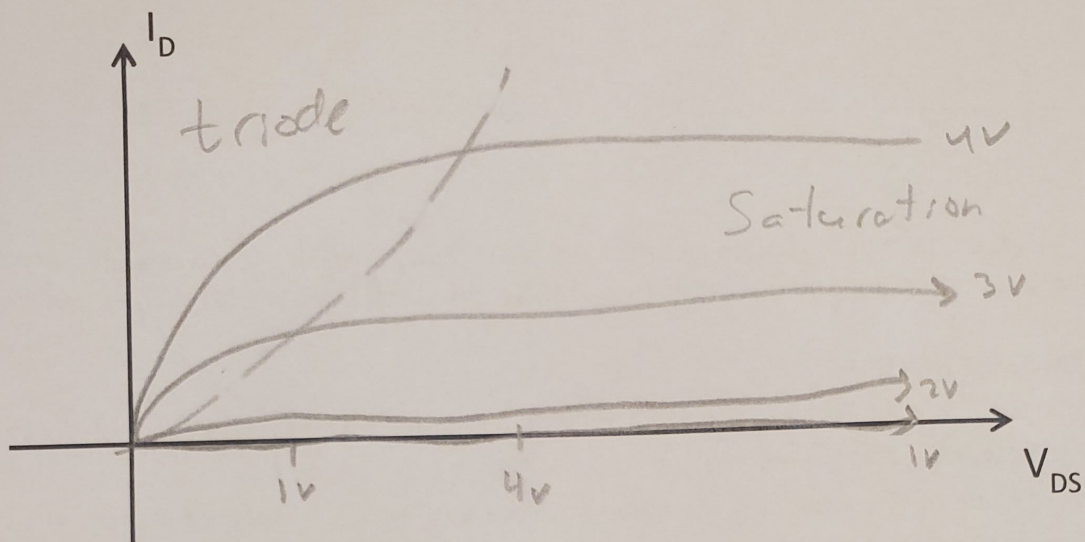

- Plot  $I_D$  vs.  $V_{DS}$  for  $V_{GS} = 1V, 2V, 3V,$  and  $4V$ .



- What is the estimated threshold voltage ( $V_t$ ) of the NMOS?

0.6V

- Based on the estimated  $V_{TN}$ , indicate the triode region and the saturation region on the graph above (use a dotted line to draw the boundary between the two regions).

Get TA's initial:

07/07

## 2. CMOS Logic Inverter

- Construct the circuit in Figure 2 below using the NMOS (2N7000) and the PMOS (TP0606). Note that Figure 1(b) applies to both NMOS and PMOS transistors.


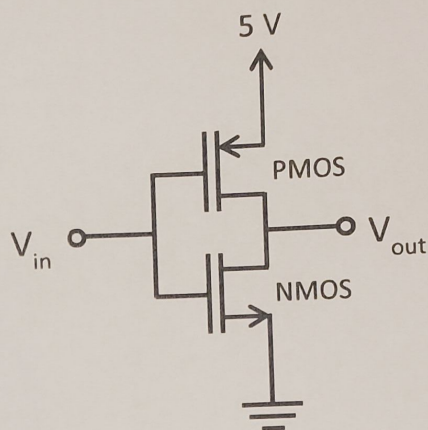


Figure 2

- Complete the following table by varying the input voltage  $V_{in}$  from 0 V to 5 V.

$V_{in}$	0V	0.5V	1V	1.5V	2V	2.5V	3V	3.5V	4V	4.5V	5V
$V_{out}$	5	5	5	5	5	4.89	4.79	4.60	4.30	4.19	4.18

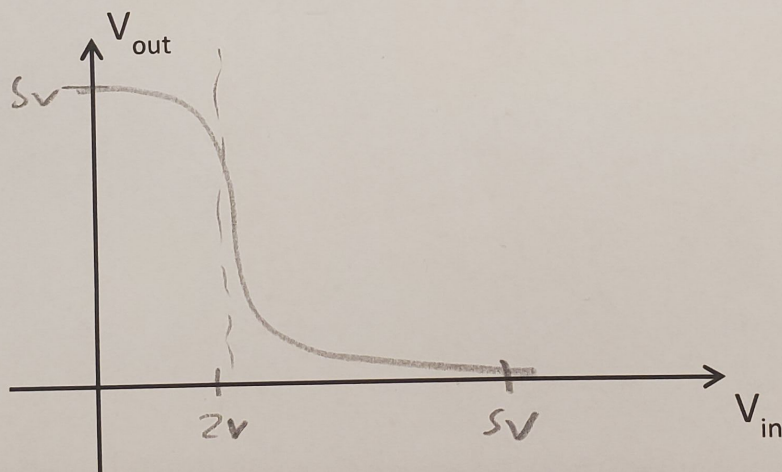- Using the data from the above table, plot the voltage transfer characteristics ( $V_{out}$  vs.  $V_{in}$ ) in the axes provided below.



- What is the estimated threshold voltage for the logic inverter?

$$V_T = 2V$$

Get TA's initial:

*[Handwritten signature]*