

ECE 541: Electric Circuits

Laboratory Exercise #3: Introduction to AC Signals

Weeks of 10/24/22 (Group A) and 10/31/22 (Group B)

Name: Nick Snyder

Date: 10/24/22

1. Introduction

In this laboratory exercise, AC signals and their measurements will be introduced. The objective of this lab is to become familiar with a signal (waveform) generator and an oscilloscope. Signal generators are capable of producing AC waveforms that are a function of amplitude, time, and frequency. The oscilloscope can display and enable measurement of voltage waveforms. Students will use both the digital multi-meter (DMM) and the oscilloscope to measure peak amplitude and RMS voltages at different points in a resistor network. The concepts of node-voltage and mesh-current equations will be applied to the test circuits.

2. Procedure

2.1. Node-Voltage Measurement

- Set up the circuit shown in Figure 1.
- Adjust the signal generator to produce a 1 V amplitude sinusoid at 1 kHz.
- Using the oscilloscope, measure the amplitude and frequency of the input waveform at node V_1 and confirm that the waveform generator is adjusted properly.
- Using the oscilloscope, measure the peak voltages at node V_2 and V_3 (relative to GND).

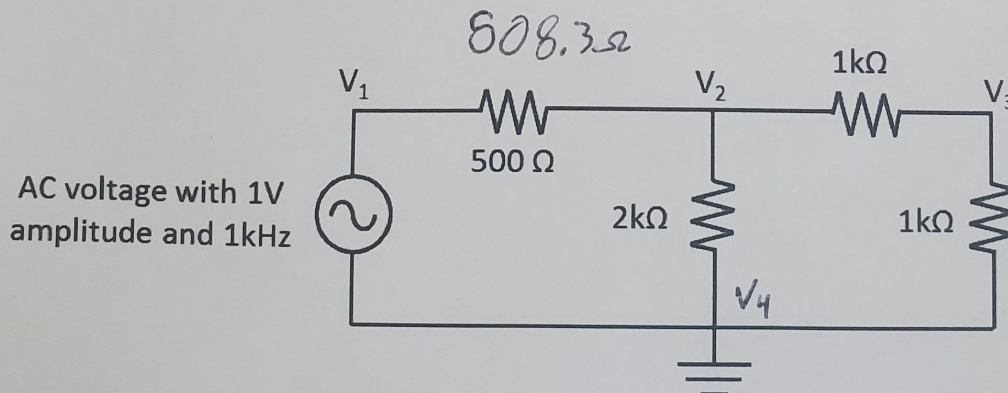


Figure 1: Resistive Circuit with Sinusoidal Waveform Input

- Record the measurements below:

$V_{1, \text{peak}}$: 1 V $V_{2, \text{peak}}$: 0.64 V $V_{3, \text{peak}}$: 0.330 V

- Using the DMM measure the RMS (Root Mean Square) voltage at nodes V_1 , V_2 , and V_3 (Relative to GND).

$V_{1, \text{RMS}}$: ~~0.6679 mV~~ $V_{2, \text{RMS}}$: 44.24 mV $V_{3, \text{RMS}}$: 22.11 mV
0.87

- Calculate the RMS voltages at nodes V_1 , V_2 , and V_3 using the amplitudes V_1 , V_2 , and V_3 . Note: For a sinusoidal waveform, $V_{\text{RMS}} = \frac{V_{\text{peak}}}{\sqrt{2}}$

$$\frac{1}{\sqrt{2}}$$

$$\frac{0.64}{\sqrt{2}}$$

$$\frac{0.33}{\sqrt{2}}$$

$V_{1, \text{RMS}}$: 0.707 V $V_{2, \text{RMS}}$: 0.453 V $V_{3, \text{RMS}}$: 0.233 V

- Do the calculated RMS voltages match the DMM-measured RMS voltages?

They are close but not exact

- Measure the frequency of the waveforms at nodes V_1 , V_2 , and V_3 .
Note: This should be done both with the DMM and from the waveform period measured on the oscilloscope.

Freq@ V_1 : 1,006 Hz Freq@ V_2 : 1006 Hz Freq@ V_3 : 1006 Hz

- Using the node-voltage equations, calculate the RMS voltages at nodes V_1 , V_2 , and V_3 .

$$\frac{V_1 - V_4}{\sqrt{2}} = \frac{1}{\sqrt{2}}$$

$$\frac{V_2 - V_4}{\sqrt{2}} = \frac{0.64}{\sqrt{2}}$$

$$\frac{V_3 - V_4}{\sqrt{2}} = \frac{0.33}{\sqrt{2}}$$

$V_{1, \text{RMS}}$: 0.707 $V_{2, \text{RMS}}$: 0.453 $V_{3, \text{RMS}}$: 0.233

- Do the node voltages calculated using the node-voltage technique equal the measured node voltages?

same

- Using the invert and add functions of the oscilloscope, measure the voltage between nodes V_2 and V_3 , that is $(V_2 - V_3)$.

$(V_2 - V_3)_{\text{peak}}$: 1.22 V

$(V_2 - V_3)_{\text{RMS}}$: 386 mV

- Using the DMM, measure the RMS voltage of $(V_2 - V_3)$.

$(V_2 - V_3)_{\text{RMS}}$: 36.83 mV

- Does the voltage $(V_2 - V_3)_{\text{RMS}}$ calculated from the oscilloscope measurements match the voltage measured with the DMM?

no

- Check your answers in section 2.1 with the TA.

TA's Signature: _____

