

# Digital Multimeter(DMM) Tutorial (Agilent U3401A)

ECE 401

Perspectives in Electrical and  
Computer Engineering


## Outlines:

- ✓ What is multimeter? What does multimeter measures?
- ✓ Multi-function description
- ✓ Multimeter connections

# What is multimeter? What does multimeter measures?


- It is an electronic instrument used to measure electric voltage, current and resistivity.
- Multimeters provide the flexibility to measure different electrical properties rather than using individual meters.

# Multi-function description

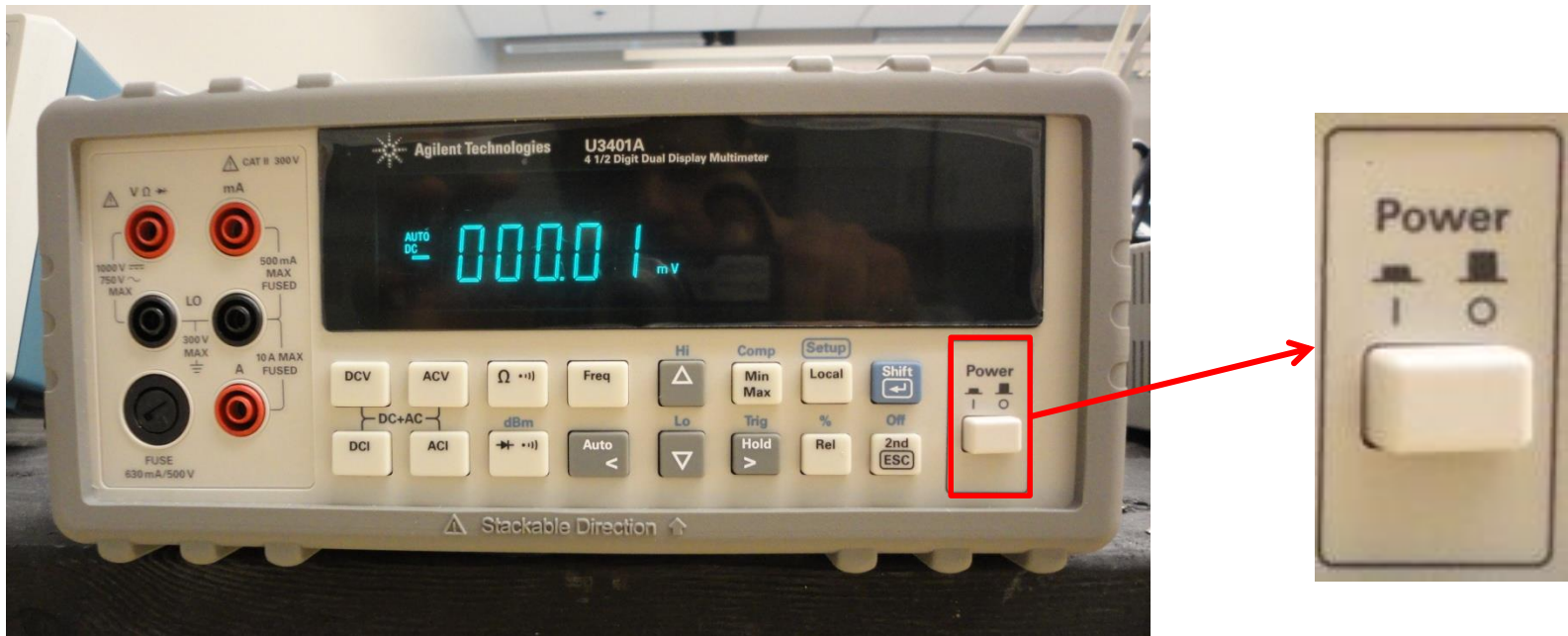


Press to power-on or power-off the U3401A multimeter.

# Multi-function description cont.

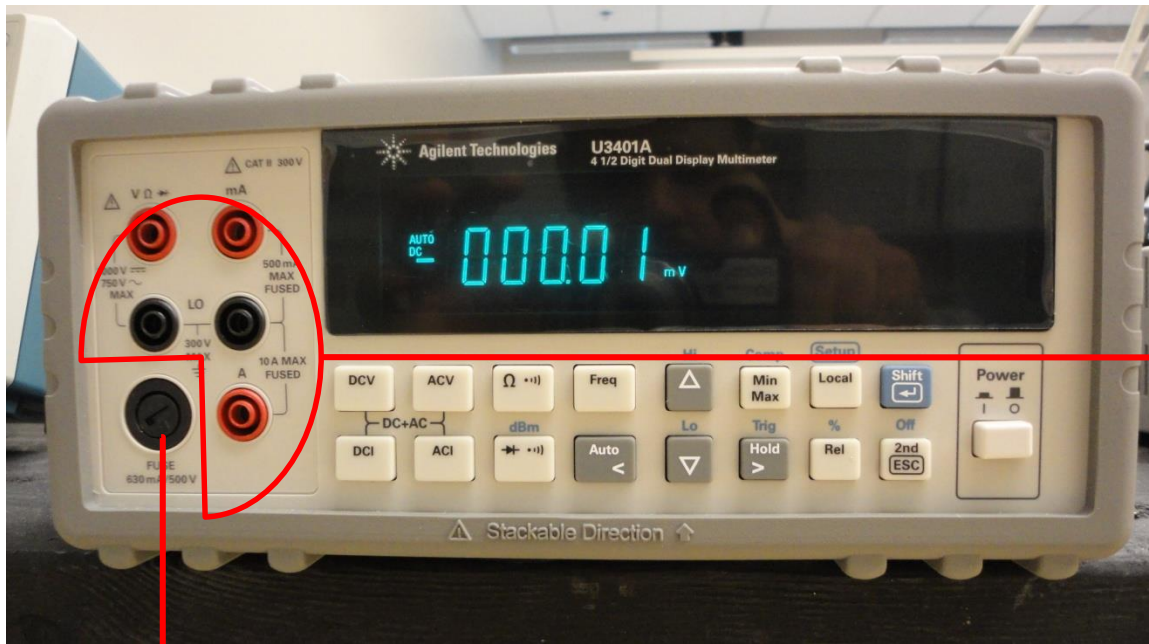


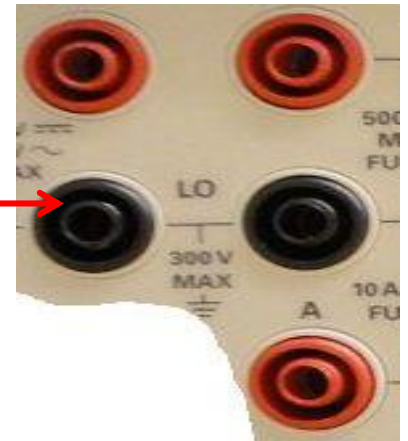Voltage, current and resistance input terminals



Fuse

## Multi-function description cont.

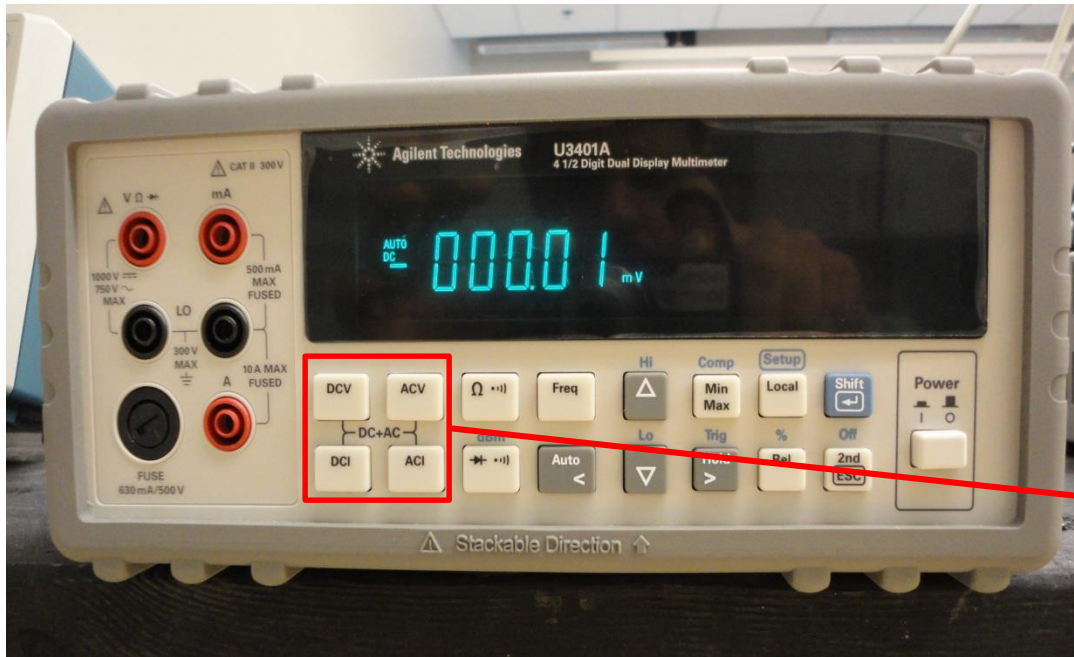

DCV

Press to select the DC voltage measurement.

ACV

Press to select the AC voltage measurement.


DCI

Press to select the DC current measurement.

ACI

Press to select the AC current measurement.

# Multi-function description cont.

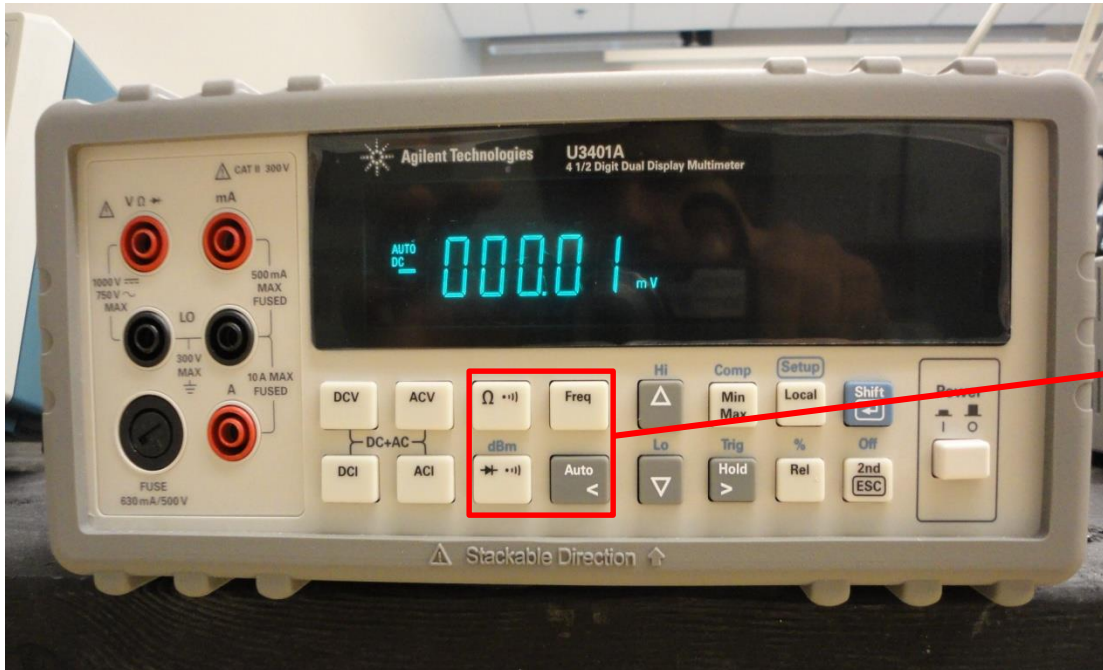

Press to select the frequency measurement.



Press to toggle between the diode and continuity measurement.



Press to toggle between resistance or resistance continuity.



Press to toggle between manual ranging and autoranging





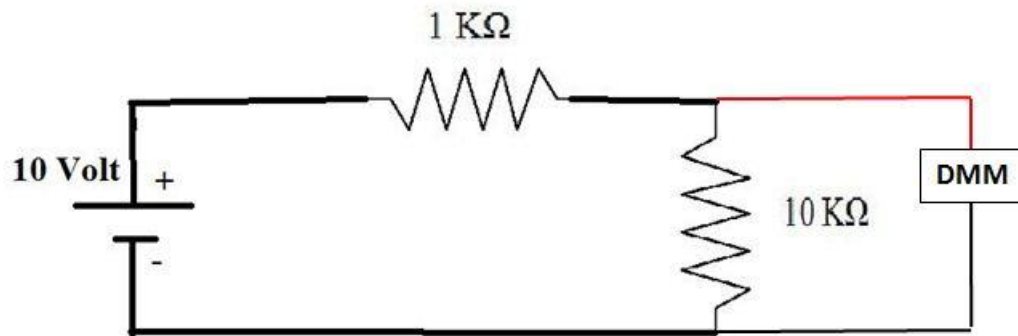
# Multimeter connections

To explain the measurement features of DMM, two resistor-based circuits are presented.

- ❑ The First circuit consists of a D.C power supply and two resistors connected in series as follows:






# Multimeter connections cont.

To measure the voltage across a particular resistor (see the illustration figure next slide):


- Connect the red probe between the DMM red voltage terminal and the positive side of the resistor in the circuit.
- Connect the black probe between the DMM black voltage terminal and the negative side of the resistor in the circuit.
- Press the pushbutton (DCV) on the DMM to read the voltage measurement across the resistor.

# Multimeter connections cont.

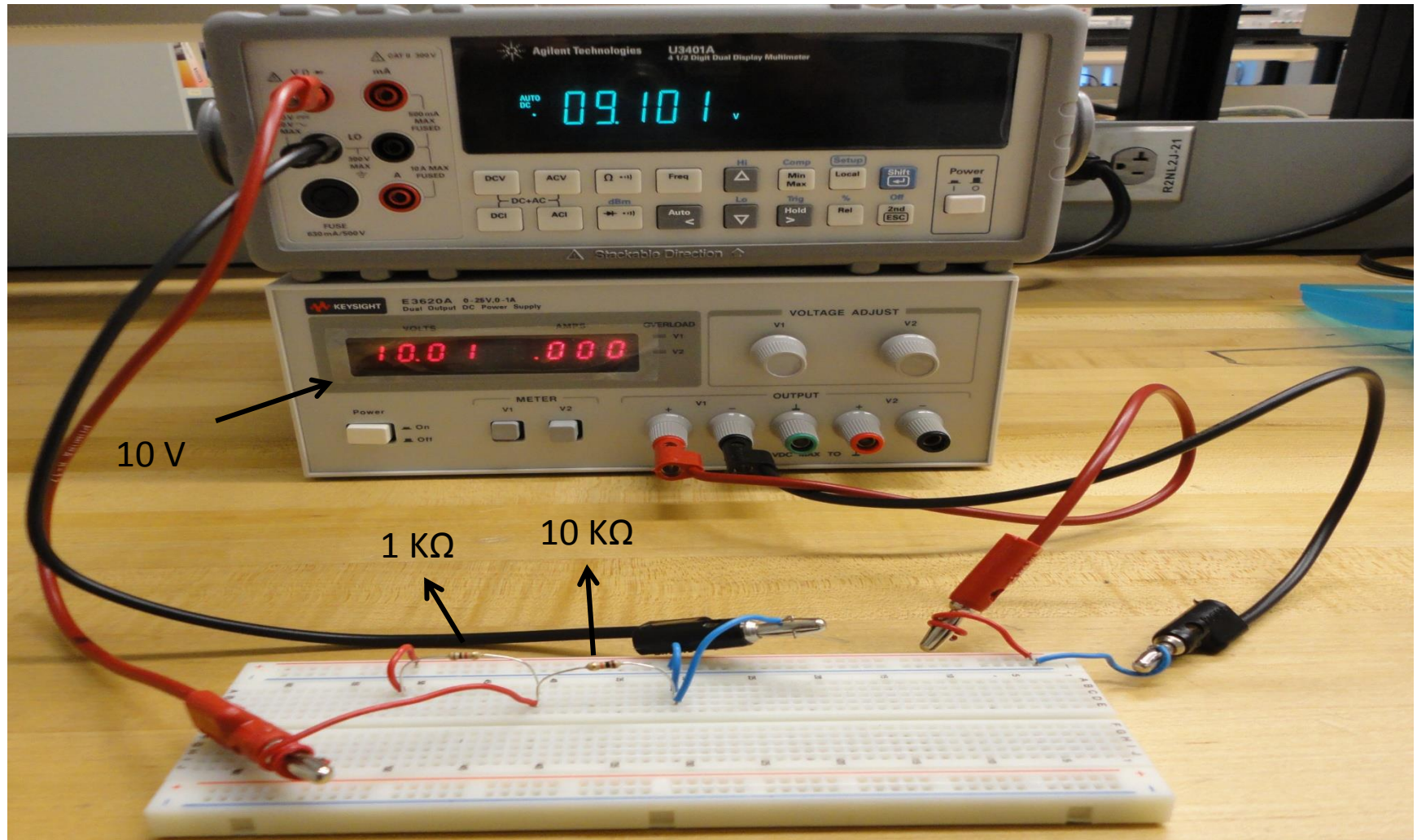

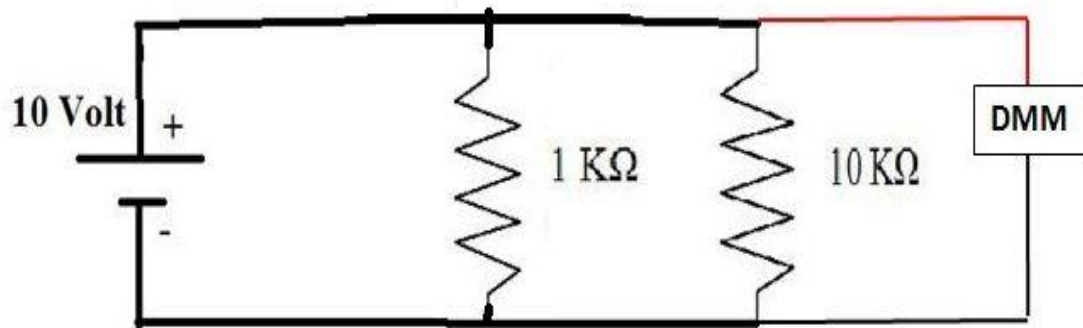
# Multimeter connections cont.

The second circuit consists of a D.C power supply and two resistors connected in parallel (as it is illustrated in next slide):



# Multimeter connections cont.

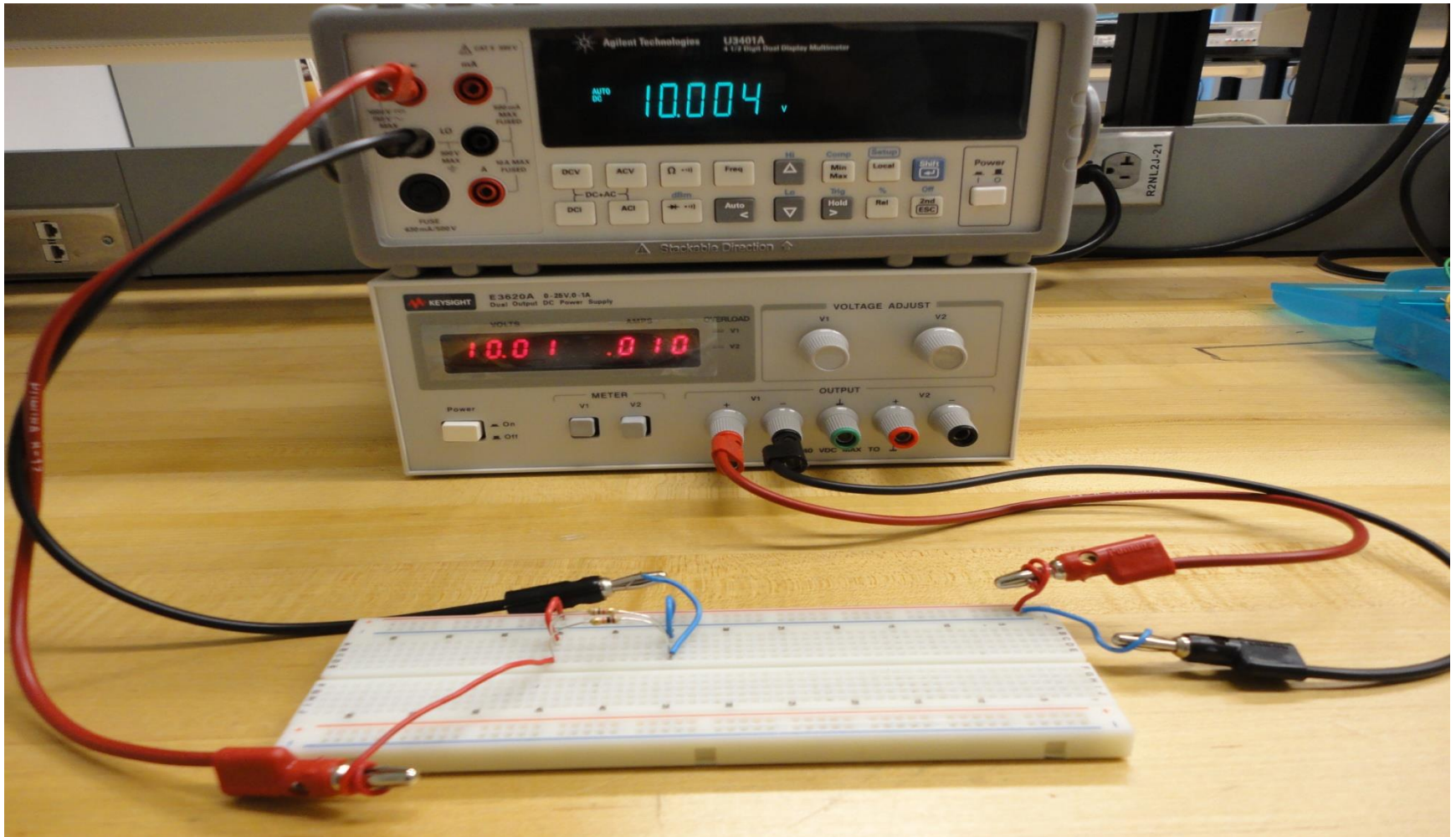



# Multimeter connections cont.

The current ( $I_R$ ) can be measured using the obtained voltages in previous circuits (series, parallel) by applying Ohm's law:

$$I_R(\text{Amp}) = \frac{V_R(\text{Volt})}{R(\Omega)}$$

Where  $V_R$  is the voltage across resistor ( $R$ )

