

TOTAL: ____/10

ECE 543: Introduction to Digital Systems

Homework #3

Due: Friday, October 1st, 2021 (6 P.M.)

Student Name: _____

Note:

- **Please use this sheet as a cover page.**
- **Your work must be hand-written (no typing please).**
- **Homework must be submitted electronically through Canvas in a PDF format.**

Do the following problems from “Fundamentals of Digital Logic with Verilog Design” by Brown & Vranesic (3rd Edition)

Solve the following problems:

Problems from Chapter 2:

2.38, 2.40

2. 38

x_1	x_2	x_3	f
0	0	0	0
0	0	1	1
0	1	0	d
0	1	1	0
1	0	0	1
1	0	1	d
1	1	0	0
1	1	1	1

	$\bar{x}_2\bar{x}_3$	\bar{x}_2x_3	$x_2\bar{x}_3$	x_2x_3
\bar{x}_1	0	1	0	d
x_1	1	d	1	0

	$\bar{x}_1\bar{x}_2$	\bar{x}_1x_2	$x_1\bar{x}_2$	x_1x_2
\bar{x}_3	0	0	0	0
x_3	0	0	0	0

$$x_1\bar{x}_2 + x_1x_3 + \bar{x}_2x_3$$

$$(\bar{x}_1 + x_2)(\bar{x}_1 + \bar{x}_3)(x_2 + \bar{x}_3)$$

40

x_1	x_2	x_3	x_4	f
0	0	0	0	1
0	0	0	1	d
0	0	1	0	1
0	0	1	1	d
0	1	0	0	0
0	1	0	1	0
0	1	1	0	d
0	1	1	1	d
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

	$\bar{x}_3\bar{x}_4$	\bar{x}_3x_4	$x_3\bar{x}_4$	x_3x_4
$\bar{x}_1\bar{x}_2$	1	d	d	1
\bar{x}_1x_2	0	0	d	d
x_1x_2	0	0	1	0
$x_1\bar{x}_2$	1	1	0	1

$$\bar{x}_2\bar{x}_4 + \bar{x}_2\bar{x}_3x_4 + x_2x_3x_4$$

$$(x_2 + x_4)(x_2 + x_3 + \bar{x}_4)(\bar{x}_2 + \bar{x}_3 + \bar{x}_4)$$