

Nicholas Snyder


ECE 401

Homework 6

Due 10/21

1 Resistive Networks

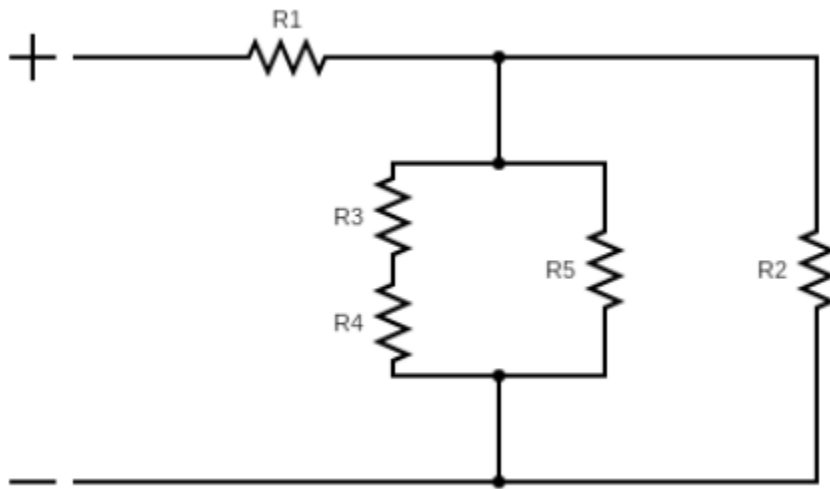Using the rules of resistances in Series and in Parallel, find the equivalent resistance, R_{eq} , of the following:



Where $R_1 = 10 \text{ k}\Omega$, $R_2 = 7.5 \text{ k}\Omega$, $R_3 = 9.1 \text{ k}\Omega$, $R_4 = 3.6 \text{ k}\Omega$, and $R_5 = 5.1 \text{ k}\Omega$.


Step 1: Reduce R_3 and R_4 to form $R_3 \parallel R_4$

$$R_3 + R_4 = R_3 \parallel R_4$$

$$9100 + 3600 = 12700$$

$$R_3 \parallel R_4 = 12.7 \text{ k}\Omega$$

Equivalent circuit:

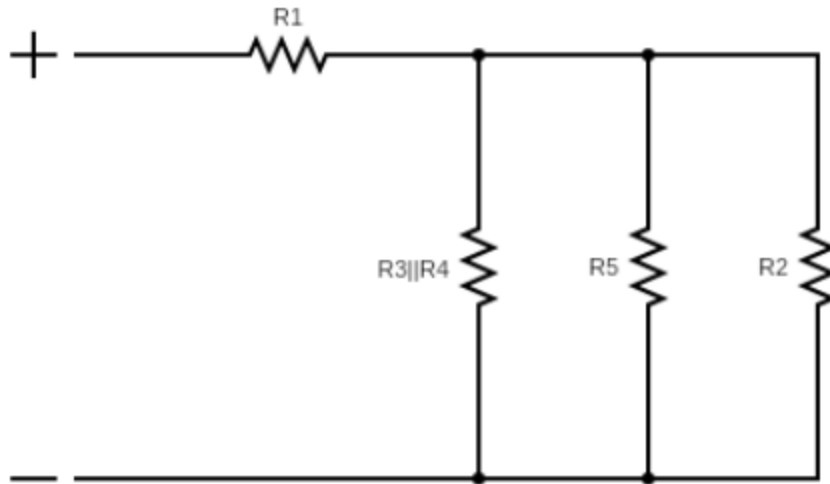


Step 2: Reduce $R3 || R4$, $R5$, and $R2$ to form $R3 || R4 || R5 || R2$

$$1 / ([1 / R3 || R4] + [1 / R5] + [1 / R2]) = R3 || R4 || R5 || R2$$

$$1 / ([1 / 12700] + [1 / 5100] + [1 / 7500]) = 2450$$

$$R3 || R4 || R5 || R2 = 2.45k\Omega$$

Equivalent circuit:

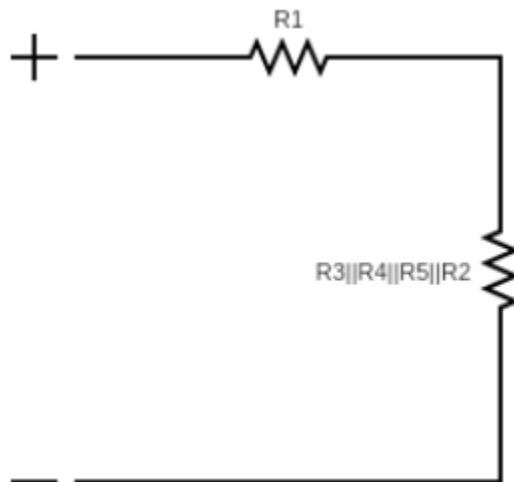


Step 3: Reduce $R3 || R4 || R5 || R2$ and $R1$ to form $R3 || R4 || R5 || R2 || R1$

$$R3 || R4 || R5 || R2 + R1 = R3 || R4 || R5 || R2 || R1$$

$$2450 + 10000 = 12450$$


$$R3 || R4 || R5 || R2 || R1 = 12.45k\Omega$$

Equivalent circuit:

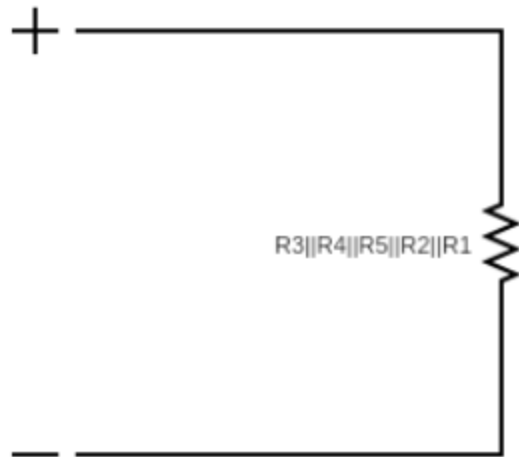

2 Ohm's Law

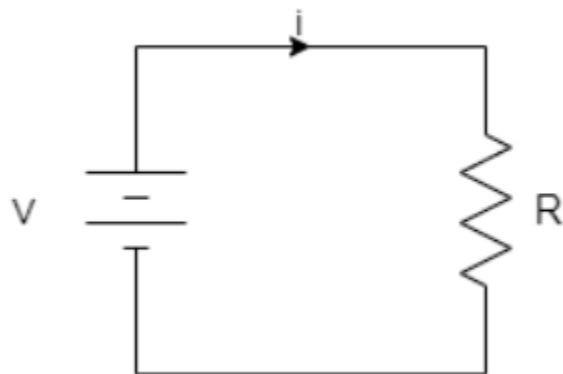Using Ohm's Law, determine the following from:



- A) The voltage, V , given that resistor has a resistance of $R = 1.8 \text{ k}\Omega$ and the current, I , is 130 mA.

$$V = I * R$$

$$0.13 * 1800 = 234$$

$$V = 234\text{V}$$

- B) The current, given that $R = 2.2 \text{ k}\Omega$ and $V = 12 \text{ V}$

$$I = V / R$$

$$12 / 2200 = 0.005454$$

$$I = 5.454 \text{ mA}$$

- C) The resistance, given that $V = 15 \text{ V}$ and $I = 3 \text{ mA}$.


$$R = V / I$$

$$15 / 0.003 = 5000$$

$$R = 5\text{k}\Omega$$

3 Circuit Analysis

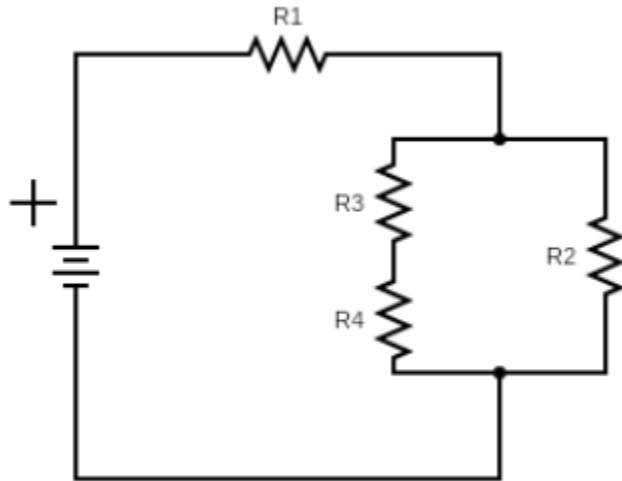The following circuit has a voltage of 20 V, $R_1 = 1.8 \text{ k}\Omega$, $R_2 = 9.1 \text{ k}\Omega$, $R_3 = 4.3 \text{ k}\Omega$, and $R_4 = 16 \text{ k}\Omega$:



A) Find the current through R_2 .


Step 1: Reduce R_3 and R_4 to form $R_3 \parallel R_4$

$$R_3 + R_4 = R_3 \parallel R_4$$

$$4300 + 16000 = 20300$$

$$R_3 \parallel R_4 = 20.3 \text{ k}\Omega$$

Equivalent circuit:

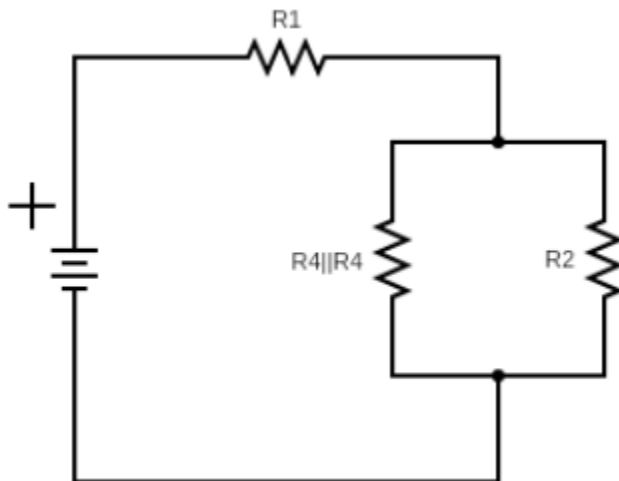


Step 2: Reduce $R_3 \parallel R_4$ and R_2 to form $R_3 \parallel R_4 \parallel R_2$

$$1 / ([1 / R_3 \parallel R_4] + [1 / R_2]) = R_3 \parallel R_4 \parallel R_2$$

$$1 / ([1 / 20300] + [1 / 9100]) = 6283$$

$$R_3 \parallel R_4 \parallel R_2 = 6.283 \text{ k}\Omega$$

Equivalent circuit:

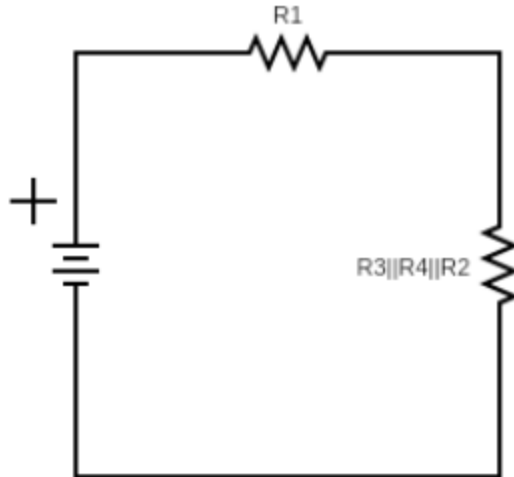


Step 3: Reduce $R3 || R4 || R2$ and $R1$ to form $R3 || R4 || R2 || R1$

$$R3 || R4 || R2 + R1 = R3 || R4 || R2 || R1$$

$$6283 + 1800 = 8083$$

$$R3 || R4 || R2 || R1 = 8.083k\Omega$$

Equivalent circuit:

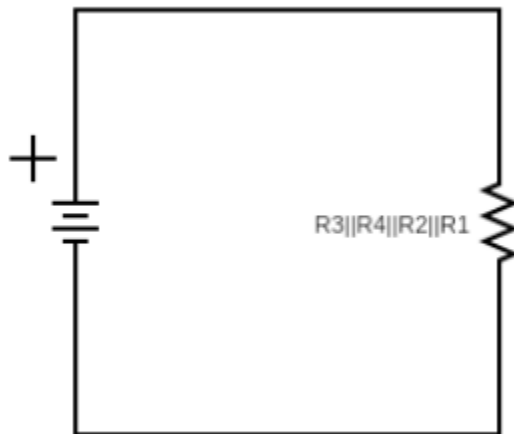

Step 4: Using Ohm's Law, find the total current through the circuit

$$I = V / R, R = R3 || R4 || R2 || R1$$

$$20 / 8083 = 0.00247$$

$$I = 2.47mA$$

Step 5: Using Ohm's Law, find the voltage drop across $R1$

$$V = I * R, V = \text{Voltage drop}, R = R1$$

$$0.00247 * 1800 = 4.446$$

$$\text{Voltage drop across } R1 = 4.446V = V_{R1}$$

Step 6: Compare the total voltage to the voltage drop across $R1$ to find $V_{R3 || R4 || R2}$

$$V - V_{R1} = V_{R3 || R4 || R2}$$

$$20 - 4.446 = 15.554$$

$$V_{R3 || R4 || R2} = 15.554$$

Step 7: From $V_{R3||R4||R2}$, find both V_{R2} and $V_{R3||R4}$

$$V_{R2} = V_{R3||R4} = V_{R3||R4||R2} / 2$$

$$15.554 / 2 = 7.777$$

$$V_{R2} = V_{R3||R4} = 7.777V$$

Step 8: Using Ohm's Law, Find the current through R2

$$I = V / R$$

$$7.777 / 9100 = 0.000854$$

$$I = 0.854mA, A \text{ is solved}$$

B) Find the voltage across R4.

Step 1: Using the information from part A and Ohm's Law, find the current through $R3 || R4$

$$I = V / R$$

$$7.775 / 20300 = 0.000383$$

$$I = 0.383mA, I_{R3||R4} = I_{R3} = I_{R4}$$

Step 2: Using Ohm's Law, find the voltage drop across R4


$$V = I * R$$

$$0.000383 * 16000 = 6.128$$

$$V_{R4} = 6.128V, B \text{ is solved}$$

4 Long Wire to a Speaker

Up until now, it has been assumed that the wire in the circuit acts as a perfect conductor. This means that it has no electrical resistance. In reality, wires do offer a small amount of resistance per unit length. For the circuit below, a speaker is connected to an audio source that produces an equivalent DC voltage of 12 V. The signal then travels through $L = 3000$ meters of wire to a 6Ω speaker. Assuming the wire has a resistance per meter of $33.2 \Omega/m$, find the output power of the speaker.

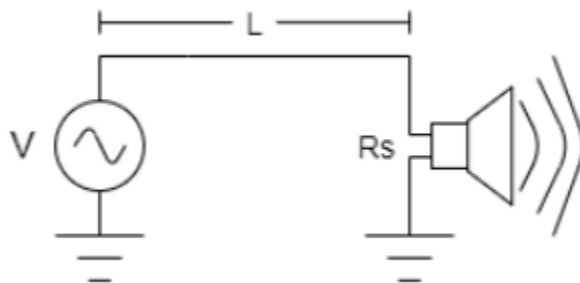

Given:

$$V_1 = 12V$$

$$R_s = 6\Omega$$

$$L_1 = 3000m$$

$$R_w = 33.2\Omega * L_1$$

$$P = I * V_1$$

Step 1: Calculate total Resistance of the wire

$$R_W = 33.2\Omega * L_1$$

$$33.2 * 3000 = 99600$$

$$R_W = 99,600\Omega$$

Step 2: Add R_W and R_S to get R_t

$$R_t = R_W + R_S$$

$$99600 + 6 = 99606$$

$$R_t = 99606\Omega$$

Step 3: Use Ohm's Law to find the current through the circuit

$$I = V_1 / R_t$$

$$12 / 99606 = 0.0001205$$

$$I = 120.5\mu A$$


Step 4: Use the Generalized Power Law to find the power of the circuit

$$P = V_1 * I$$

$$12 * 0.0001205 = 0.001446$$

$$P = 1.45mW, \text{ solved}$$

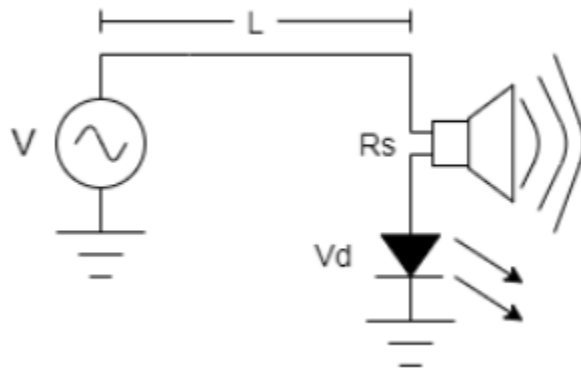To make the speaker more visible, an Light-Emitting Diode (LED) is placed following the speaker. The voltage drop across the LED, V_d , is 0.7 V. What is the new output power of the speaker?



Step 1: Using Ohm's Law, find the new total resistance

$$R_{t \text{ new}} = R_{t \text{ old}} + V_d / I$$

$$99606 + 0.7 / 0.0001205 = 105415$$

$$R_{t \text{ new}} = 105,415\Omega$$

Step 2: Use Ohm's Law to find the current through the circuit

$$I = V_1 / R_{t \text{ new}}$$

$$12 / 105415 = 0.0001138$$

$$I = 113.8\mu A$$

Step 3: Step 4: Use the Generalized Power Law to find the power of the circuit

$$P = V_1 * I$$

$$12 * 0.0001138 = 0.001366$$

$$P = 1.37mA, \text{ solved}$$