

TOTAL: ____/10

ECE 543: Introduction to Digital Systems

Homework #2

Due: Friday, September 24th, 2021 (6 P.M.)

Student Name: _____

Note:

- **Please use this sheet as a cover page.**
- **Your work must be hand-written (no typing please).**
- **Homework must be submitted electronically through Canvas in a PDF format.**

Do the following problems from “Fundamentals of Digital Logic with Verilog Design” by Brown & Vranesic (3rd Edition)

Solve the following problems:

Problems from Chapter 2:

2.37, 2.54, 2.55

2.37

x_1	x_2	x_3	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

$$\bar{x}_1 \bar{x}_2 x_3 + \bar{x}_1 x_2 \bar{x}_3 + \bar{x}_1 x_2 x_3 + x_1 \bar{x}_2 x_3$$

$$\bar{x}_1 x_3 + \bar{x}_1 x_2 \bar{x}_3 + x_1 \bar{x}_2 x_3$$

$$\bar{x}_2 x_3 + \bar{x}_1 x_2 \quad \text{SOP}$$

$$\bar{x}_1 \bar{x}_2 \bar{x}_3 + x_1 \bar{x}_2 \bar{x}_3 + x_1 x_2 \bar{x}_3 + x_1 x_2 x_3$$

$$\bar{x}_2 \bar{x}_3 + x_1 x_2$$

$$\bar{x}_2 \bar{x}_3 + x_1 x_2$$

$$\text{POS} \quad (x_2 + x_3)(\bar{x}_1 + \bar{x}_2)$$

$$\Sigma m(3, 4, 6, 7)$$

$$\bar{x}_1 x_2 x_3 + x_1 \bar{x}_2 \bar{x}_3 + x_1 x_2 \bar{x}_3 + x_1 x_2 x_3$$


$$x_2 x_3 + x_1 \bar{x}_3$$

2.54

	$x_2 x_3$	$x_2 \bar{x}_3$	$\bar{x}_2 x_3$	$\bar{x}_2 \bar{x}_3$
\bar{x}_1	1	0	0	0
x_1	1	1	0	1

	$x_1 x_3$	$x_1 \bar{x}_3$	$\bar{x}_1 x_3$	$\bar{x}_1 \bar{x}_3$
\bar{x}_2	0	1	0	0
x_2	1	1	1	0

	$x_1 x_2$	$x_1 \bar{x}_2$	$\bar{x}_1 x_2$	$\bar{x}_1 \bar{x}_2$
x_3	1	1	0	0

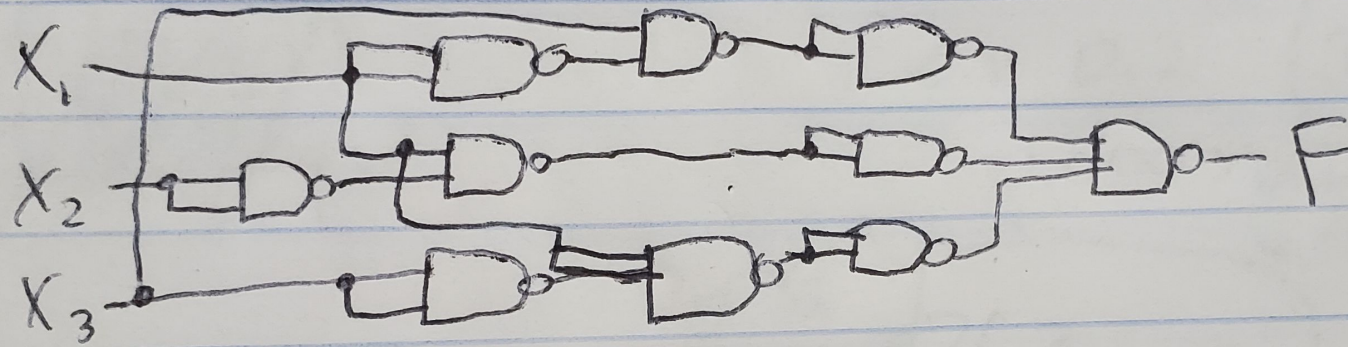

$$\bar{X}_1 X_3 + X_1 X_2 + X_1 \bar{X}_3$$