

Lab 4: Rectifier Circuits

Name: Nick SnyderMajor: CEObjective:

- To build a half-wave and a full-wave rectifier and verify the voltage waveform.
- Measure the conduction interval and verify with the theoretical values.

1. Half-Wave Rectifier

- Construct the circuit in Figure 1. Using a function generator, produce a sine wave at $V_s(t)$ with 100 Hz frequency and 5 V amplitude. Use channel 1 of oscilloscope to display V_s and channel 2 to display V_o on the scope.


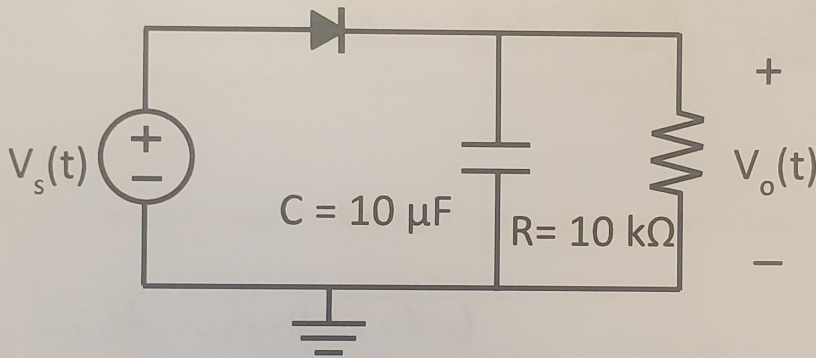


Figure 1

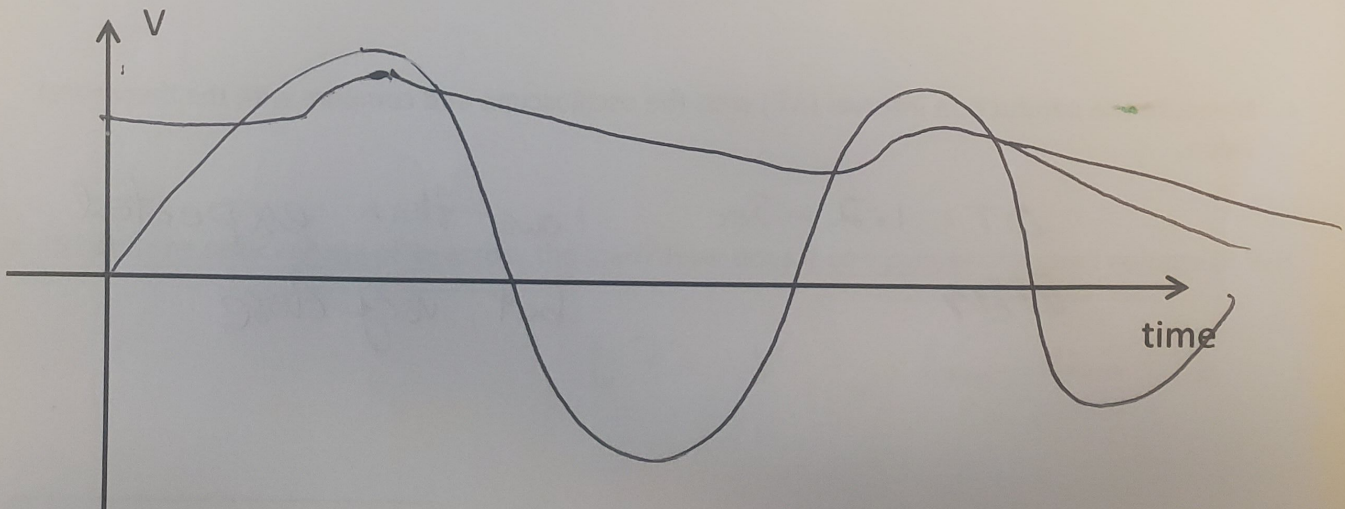- Plot two periods of V_s and V_o on the axis provided below.



- Calculate the maximum and the minimum voltage for $V_o(t)$.

$$V_{max} \left(\frac{0.01}{10000 \cdot 0.00001} \right)$$

$$0.19V$$

$$V_p - V_{th} = 2.5 - 0.6 = 1.9V = V_{max}$$

$$V_{max} - V_r = 1.9 - 0.19 = 1.71V = V_{min}$$

- Calculate the conduction interval (ΔT) and the conduction angle (θ_c)

$$\theta_c = \cos^{-1} \left(1 - \frac{V_r}{V_p} \right) = \cos^{-1} \left(1 - \frac{0.19}{2.5} \right) = 1.328 \text{ rad}$$

$$\Delta T = \frac{1.328}{100} = 1.328 \text{ msec}$$

$$\theta_c = \cos^{-1} \left(1 - \frac{1.9}{2.5} \right) = 1.328 \text{ rad}$$

$$\Delta T = \frac{1.328}{100} = 1.328 \text{ msec}$$

- Measure the maximum and minimum voltages at $V_o(t)$ and compare them with the theoretical values.

$$max: 2.13V$$

$$min: 1.96V$$

both higher than expected

- Measure the conduction interval (ΔT) with the oscilloscope and compare with the theoretical value.

$$\Delta T: 1.2 \text{ mSec}$$

~~1.2~~

lower than expected

but very close

Get TA's initial:

4/11

2. Full-Wave Bridge Rectifier

- Construct the circuit in Figure 2. Using a function generator, produce a sine wave at $V_s(t)$ with 100 Hz frequency and 5V amplitude. Connect channel 1 of oscilloscope to one end of the load resistor R_L (to measure V_1) and channel 2 to the other end (to measure V_2).


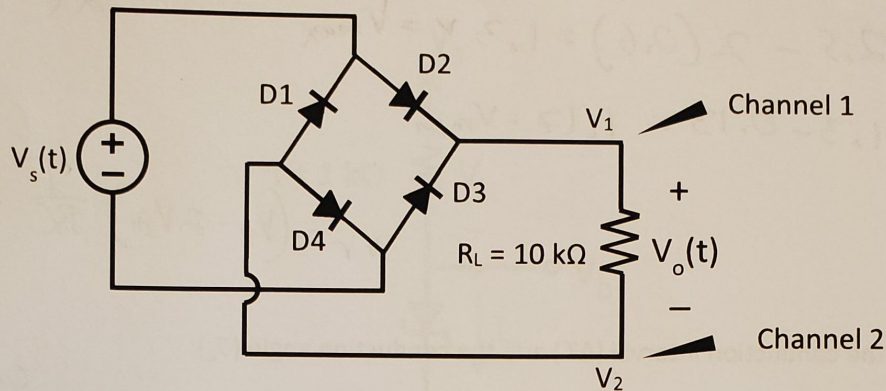


Figure 2

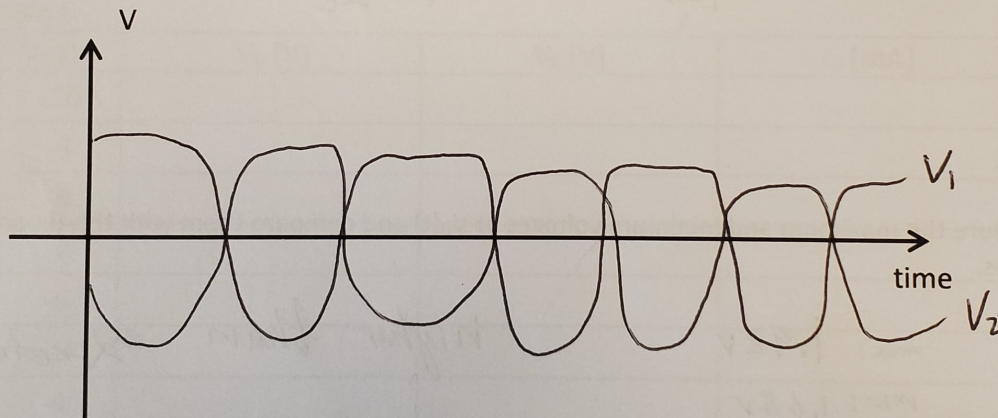- Display $V_1 - V_2$ on the oscilloscope by "adding" channel 1 and inverse of channel 2. Plot several periods of the resultant waveform on the axis provided below.



- What is the peak voltage of V_o across the load? How does it compare to the peak voltage of V_s ?

1.72 V , lower than V_s

- Now add a $10\ \mu\text{F}$ capacitor in parallel with the load resistor to obtain a crude DC voltage with a ripple.

- Calculate the maximum and the minimum voltage for $V_o(t)$.

$$2.5 - 2(0.6) = 1.3\ \text{V} = V_{\max}$$

$$1.3 - 0.13 = 1.17 = V_{\min}$$

$$5 - 2(0.6) = 3.8$$

$$0.38$$

$$V_r = (V_p - 2V_{th}) \frac{T}{RC} = 0.13\ \text{V}$$

- Calculate the conduction interval (ΔT) and the conduction angle (θ_c)

$$\cos^{-1}\left(1 - \frac{0.38}{5}\right) = \cancel{0.324} \text{ rad} = 0.34 \text{ rad}$$

$$\theta_c = \cos^{-1}\left(1 - \frac{0.13}{2.5}\right) = 0.324 \text{ rad}$$

$$\Delta T = \frac{0.324}{100} = 3.24 \text{ msec}$$

- Measure the maximum and minimum voltages at $V_o(t)$ and compare them with the theoretical values.

$$\text{max: } 1.92\ \text{V}$$

$$\text{min: } 1.68\ \text{V}$$

higher than expected

- Measure the conduction interval (ΔT) with the oscilloscope and compare with the theoretical value.

$$\cancel{2.5 \text{ msec}}$$

lower than expected

$$0.8 \text{ msec}$$

4/11