Connect diode and trans.

connect resistor

Half-wave

Turn on oscill.

plug in trans an RG-6

zoom out on oscill.

take pic

turn off trans.

add capacitor to make HWR w/ smoothing cap.

plug back in ←

(didn't get anything) ⤸

Fix knobs

~~take pic~~

make FW~~W~~R

add Diode, remove capacitor

take pic

~~make~~ add Capacitor

take pic

make bridge rect.

take pic

wrong

check connections

unplug trans.

add capacitor

take pic

clean up

Make HWR
   add voltage regulator
turn on oscil.
   take pic
Make FWR
   take pic
Make BR
   take pic

Clean up
turn off oscil ~~and trans~~
   unplug trans.